

Analog IC Design

Lecture 16 OTA Frequency Compensation

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \text{ or } V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
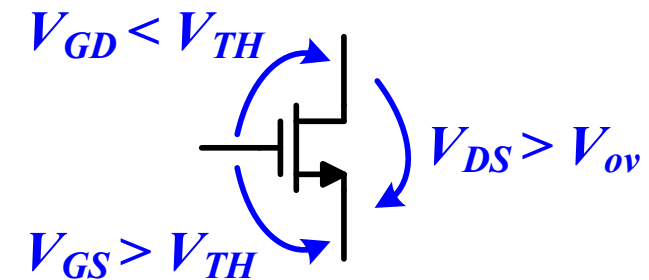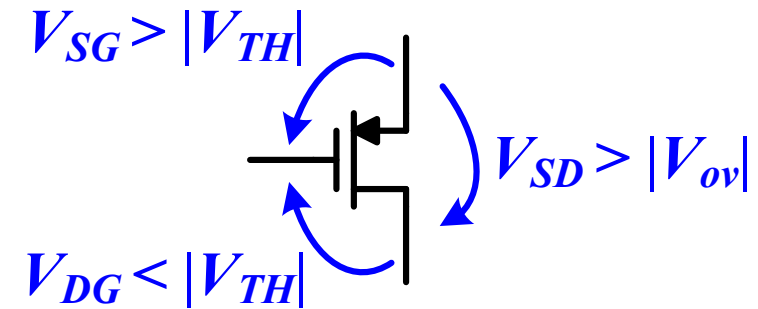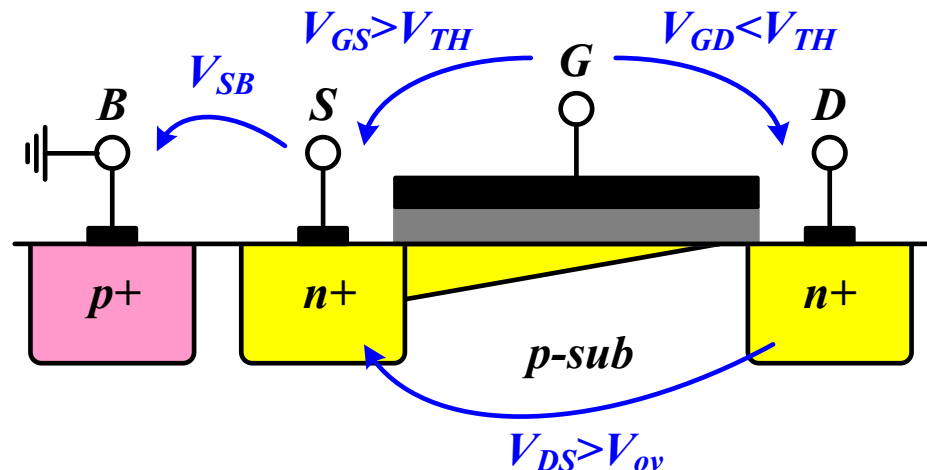
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

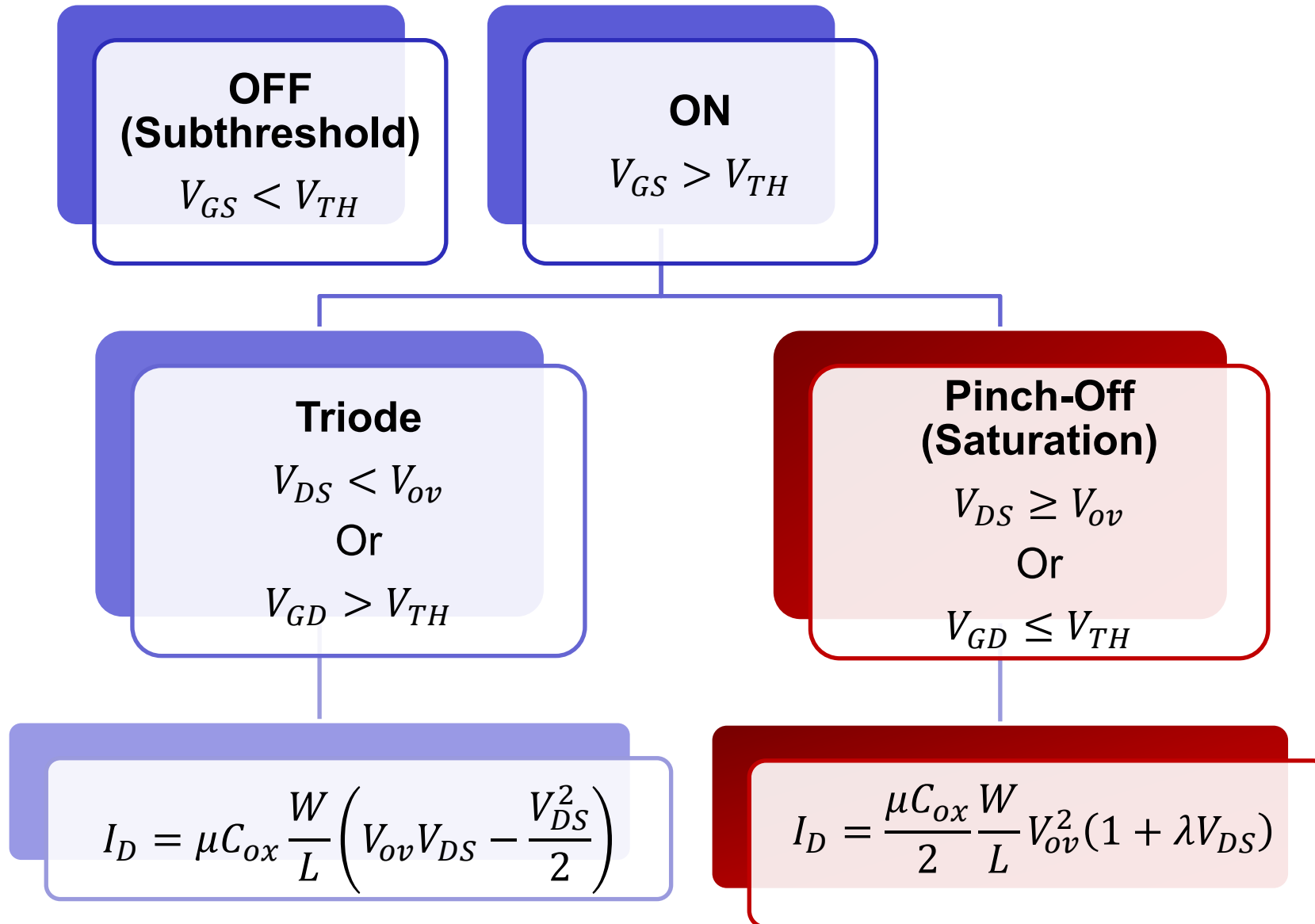

High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m$$

$$\eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$


$$V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L}$$

$$V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

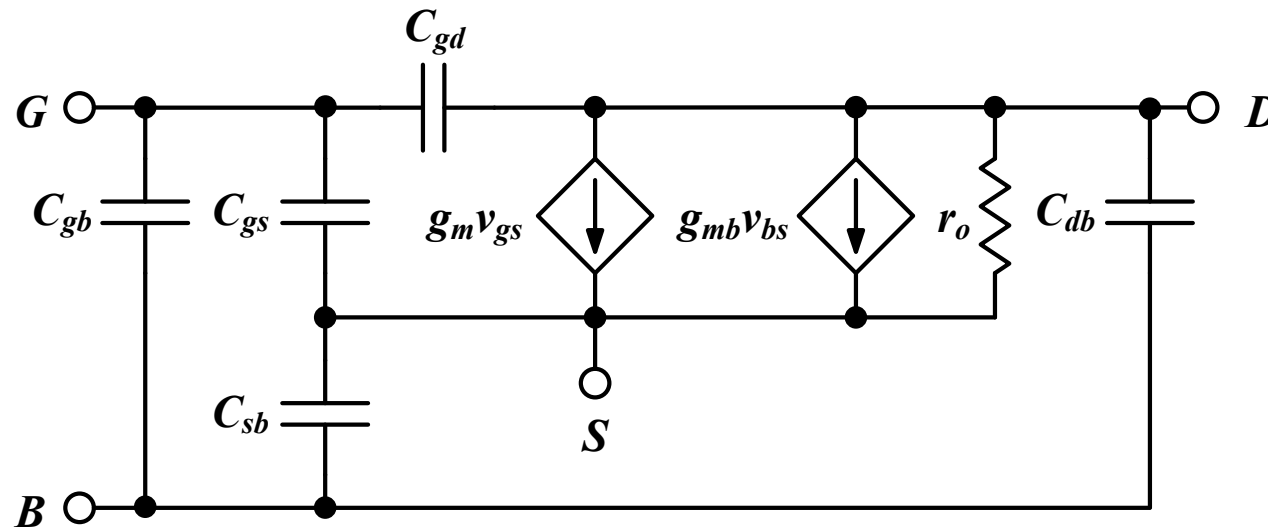

Rin/out Shortcuts Summary

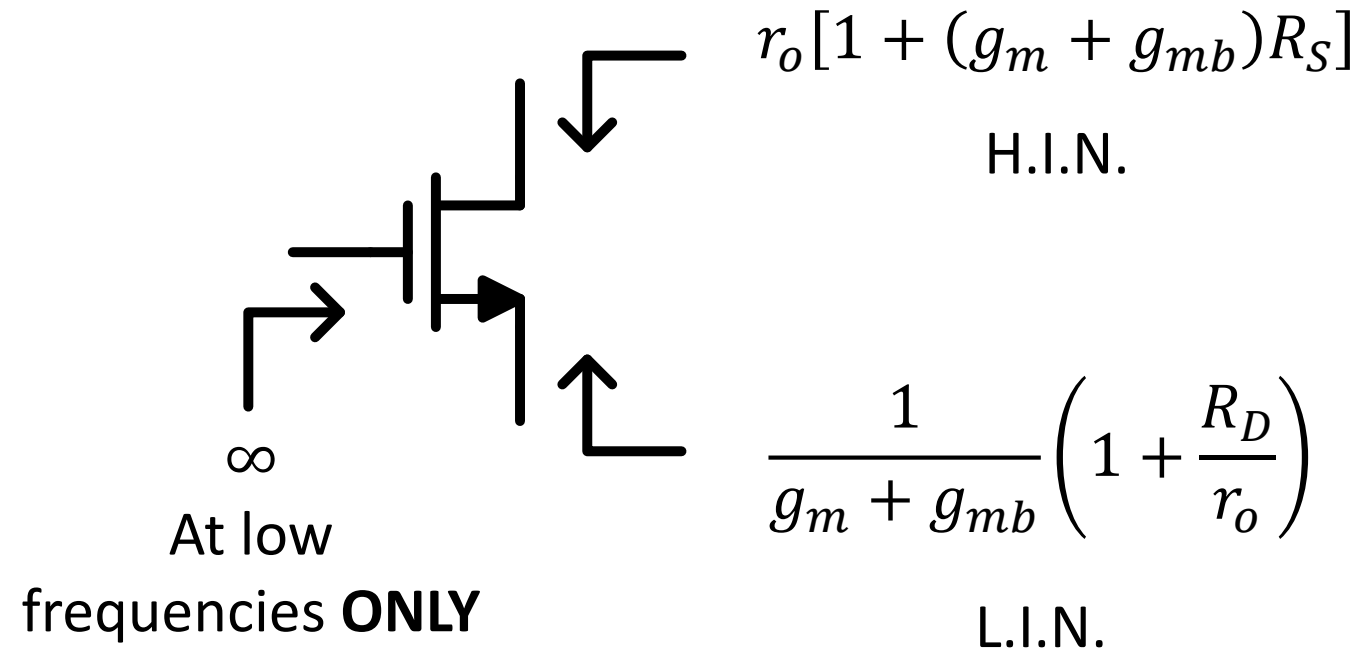

Summary of Basic Topologies

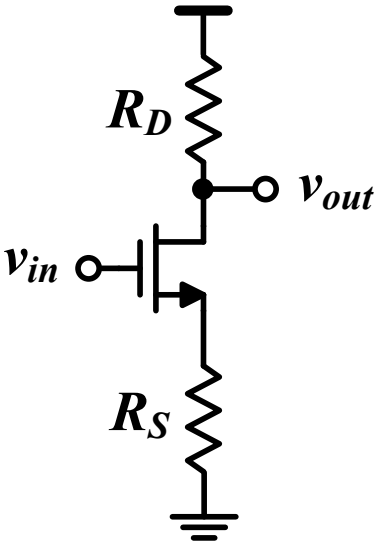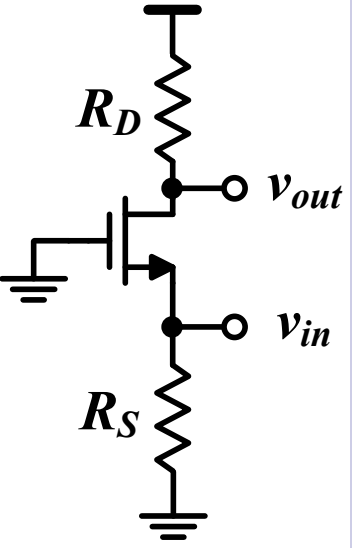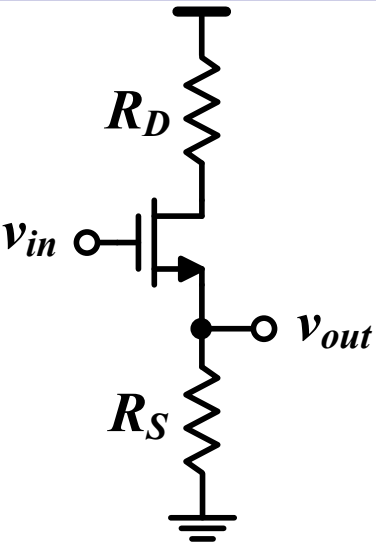	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
R_{in}	∞	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
R_{out}	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
G_m	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Differential Amplifier



	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ R_{SS})
A_{vd}	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
A_{vCM}	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
A_{vd}/A_{vCM}	1	∞	$2(g_m + g_{mb})R_{SS} \gg 1$

$$A_{vCM2d} = \frac{v_{od}}{v_{iCM}} \approx \frac{\Delta R_D}{2R_{SS}} + \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}}$$

$$CMRR = \frac{A_{vd}}{A_{vCM2d}}$$







Op-Amp

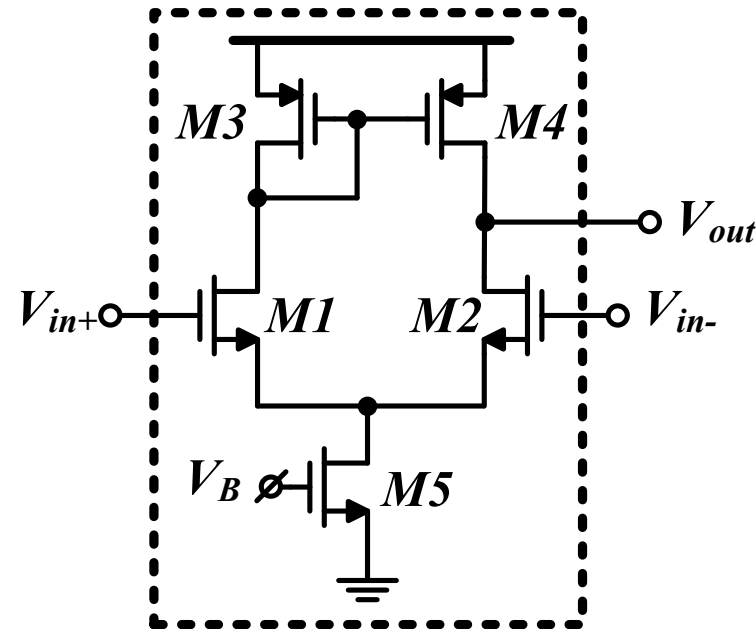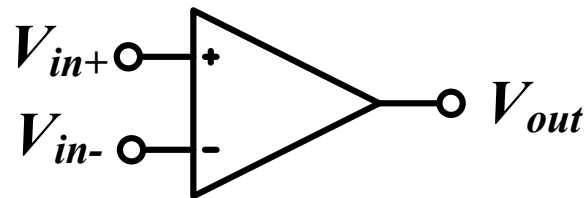- ❑ An op-amp is simply a high gain differential amplifier
 - The gain can be increased by using cascodes and multi-stage amplification
- ❑ The diff amp is a key block in many analog and RF circuits
 - DEEP understanding of diff amp is ESSENTIAL



Op-Amp vs OTA

- ❑ In short, an OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both

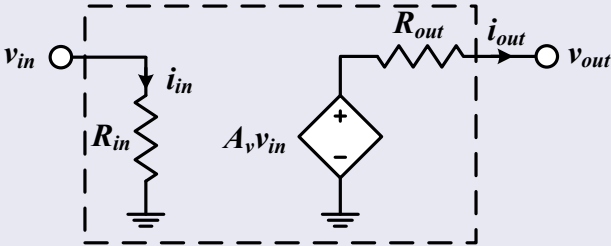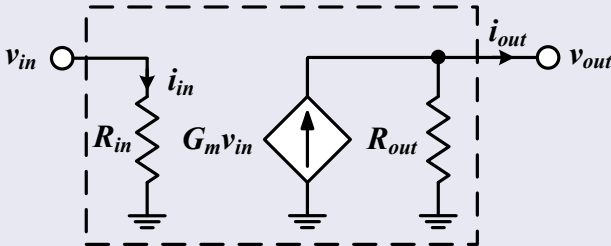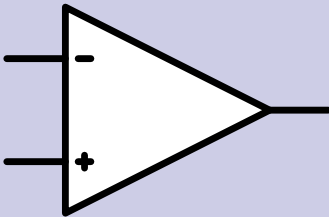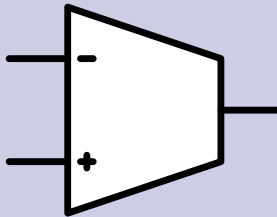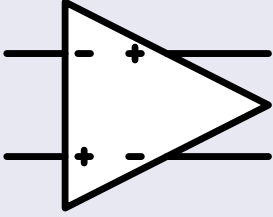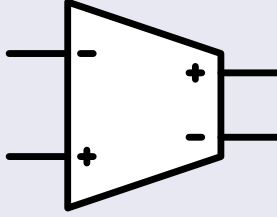	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

V-star (V^*)

- V-star (V^*) is inspired by V_{ov} but calculated from actual simulation data

$$g_m = \frac{2I_D}{V^*} \leftrightarrow V^* = \frac{2I_D}{g_m} = \frac{2}{g_m/I_D}$$

- Figures-of-merit in terms of V^*

$$g_m r_o = \frac{2I_D}{V^*} \cdot \frac{1}{\lambda I_D} = \frac{2}{\lambda V^*}$$

$$f_T = \frac{g_m}{2\pi C_{gg}} = \frac{1}{2\pi} \cdot \frac{2I_D}{V^*} \cdot \frac{1}{C_{gg}}$$

$$\frac{g_m}{I_D} = \frac{2}{V^*}$$

- The boundary between weak and strong inversion ($n = 1.2 \rightarrow 1.5$)



$$V_{ov}(SI) = V^*(WI) = 2nV_T \approx 60 \rightarrow 80mV$$

Negative Feedback

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{A_{OL}}{1 + \beta A_{OL}} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$
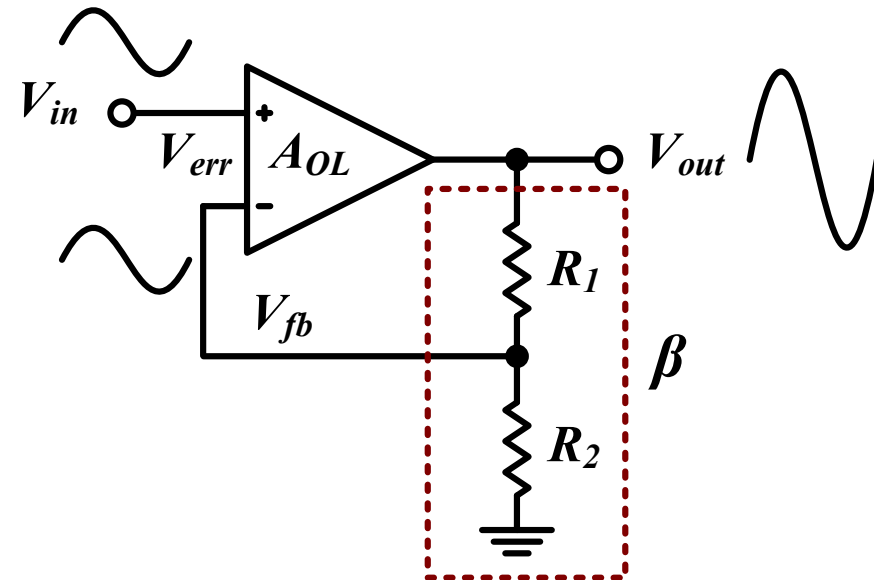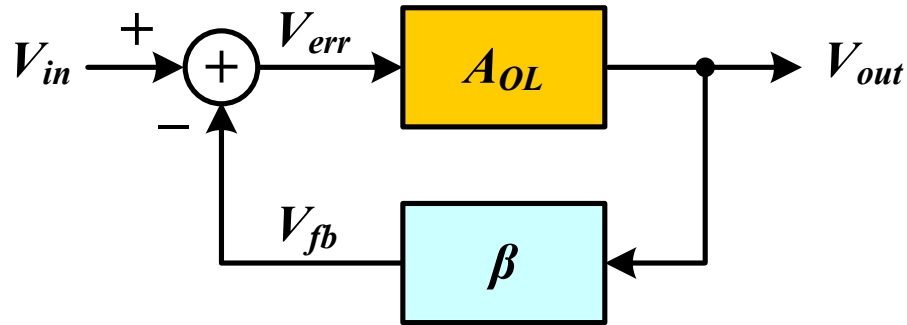
$$\omega_{p,CL} = (1 + \beta A_{OLo})\omega_{P,OL}$$




Outline

- ❑ Recapping previous key results
- ❑ **Frequency compensation**
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

Phase Margin and the Ultimate GBW


- If $\omega_{p2} = \omega_u$: PM = 45°
 - Typically inadequate (peaking/ringing)
- Thus ω_{p2} should be $> \omega_u \rightarrow \omega_{p1} \ll \omega_u < \omega_{p2}$
 - ω_{p1} defines OL BW and ω_{p2} defines ultimate GBW (max CL BW)

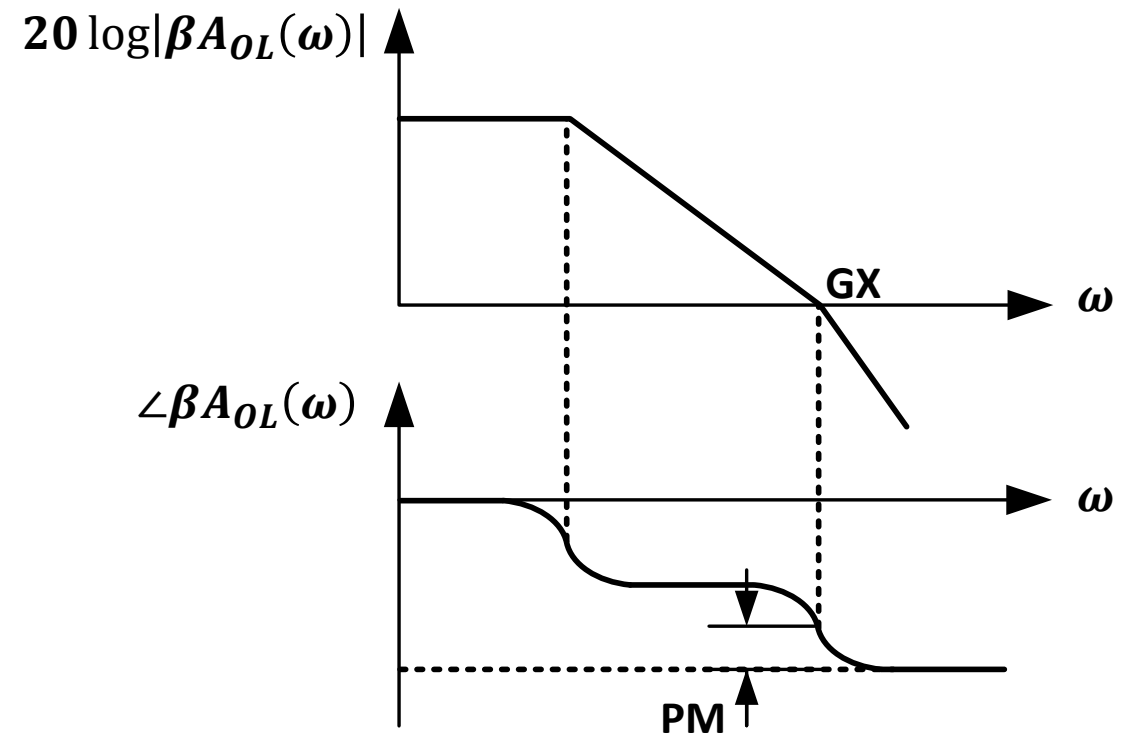Frequency domain peaking
→ noise amplification
Time domain ringing
→ poor settling time




Frequency Compensation

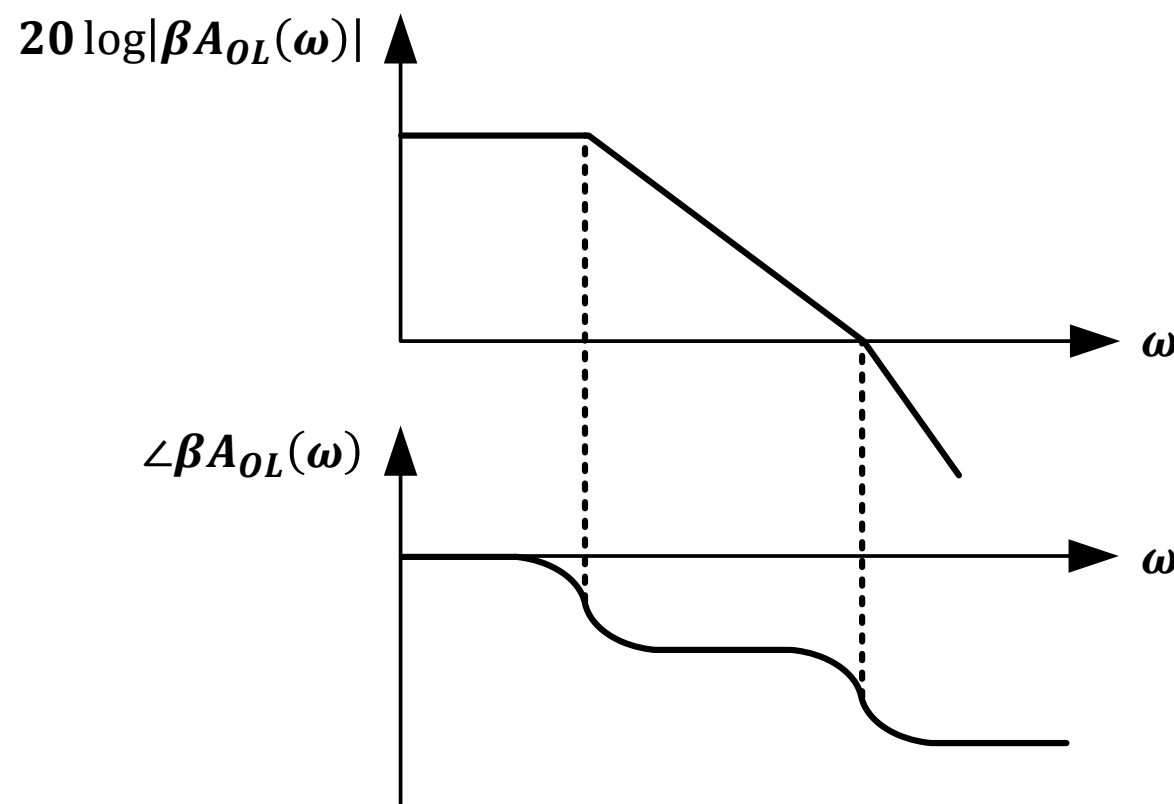- ❑ Frequency compensation: Modify the system to achieve a specific PM to control frequency domain peaking and time domain ringing
- ❑ $G_X < P_X$ is not enough: We actually need $\omega_u < \omega_{p2}$




Frequency Compensation

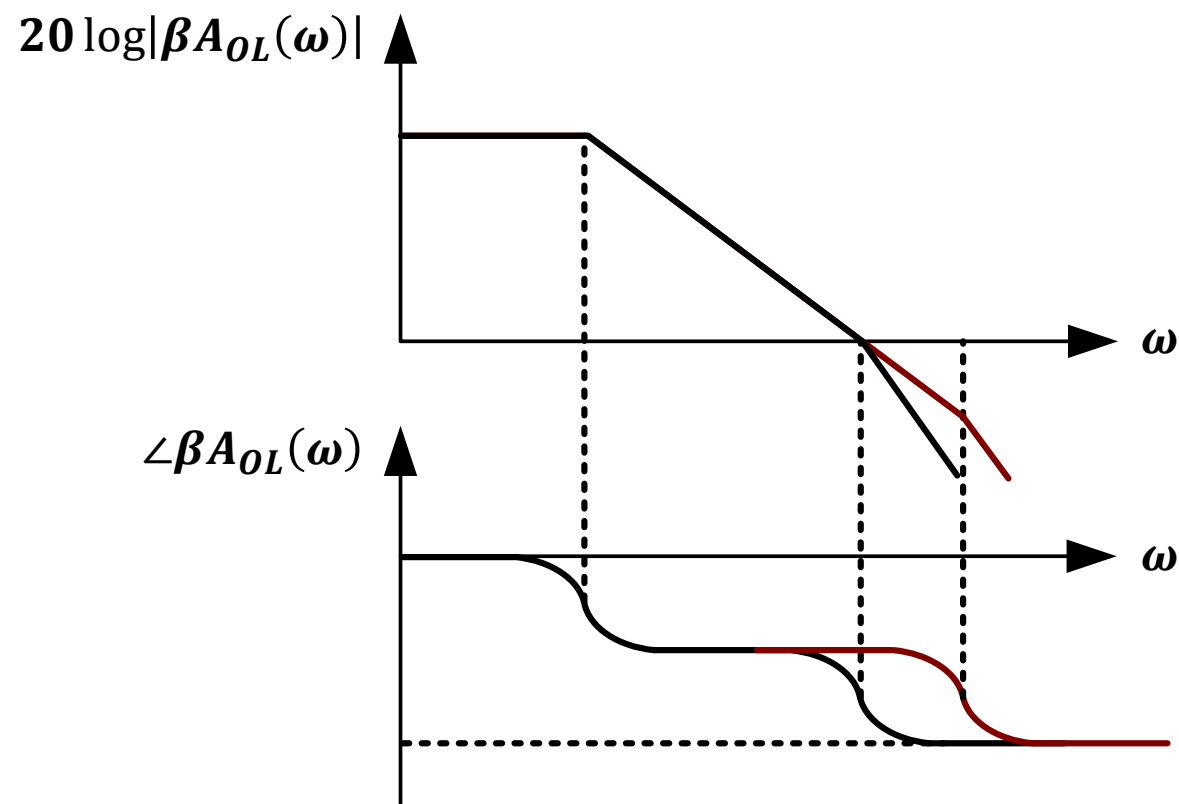- We need $G_X < P_X$ (actually $\omega_u < \omega_{p2}$)
 - Push ω_{p2} **outwards**: lower resistance/capacitance
 - Not always feasible for free



Frequency Compensation

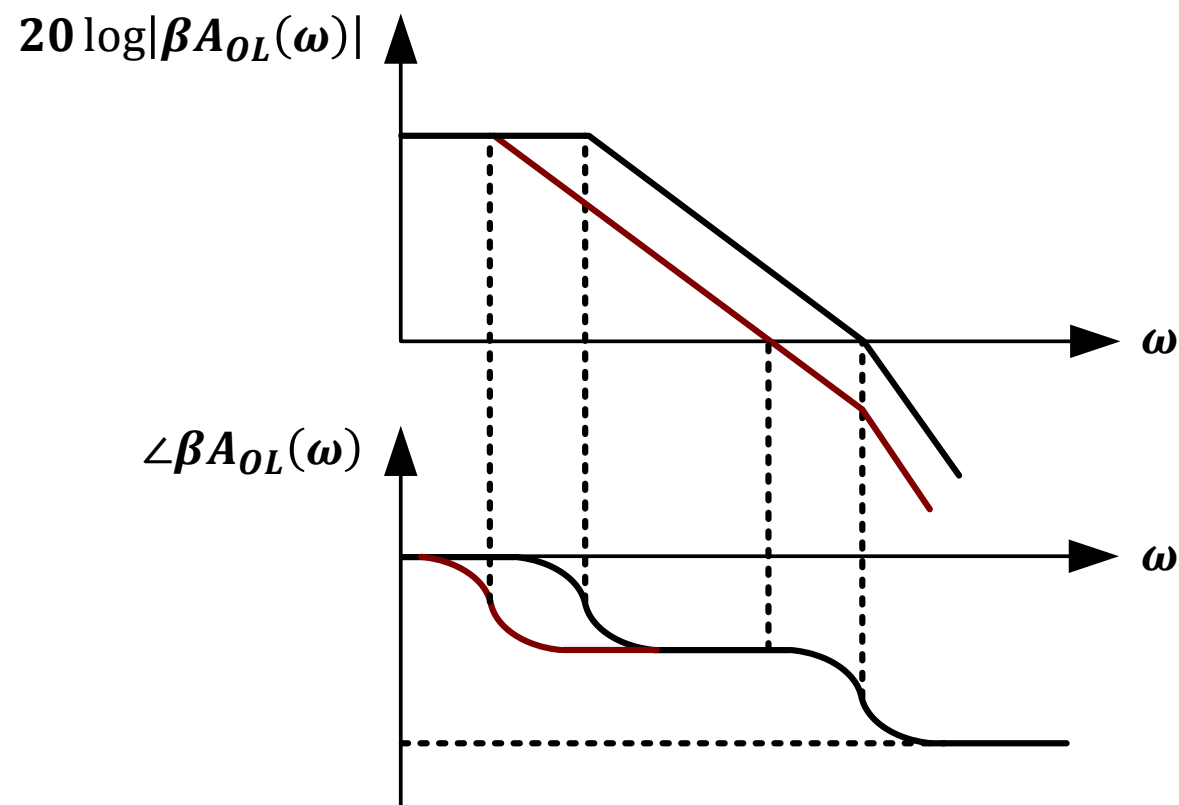- We need $G_X < P_X$ (actually $\omega_u < \omega_{p2}$)
 - Push $G_X / \omega_u / \omega_{p1}$ **inwards**: lower GBW



Compensation of Popular OTA Topologies

- ❑ Single-stage OTAs
 - 5T OTA
 - Telescopic cascode OTA
 - Folded cascode OTA
- ❑ Two-stage OTA
- ❑ Three-stage OTA
- ❑ Gain boosted OTA

Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

5T OTA

- $\omega_{p1} \ll \omega_u < \omega_{p2}$
- The H.I.N. sets BW_{OL}


$$\omega_{p1} = \omega_{pout} \approx \frac{1}{R_{out}C_{out}}$$

- The first non-dominant pole (mirror node) sets the ultimate GBW
 - Ultimate CL bandwidth (buffer)

$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m3}}{C_M} \sim \frac{\omega_T}{3}$$


- LHP zero:

$$\omega_z = 2\omega_{p2}$$

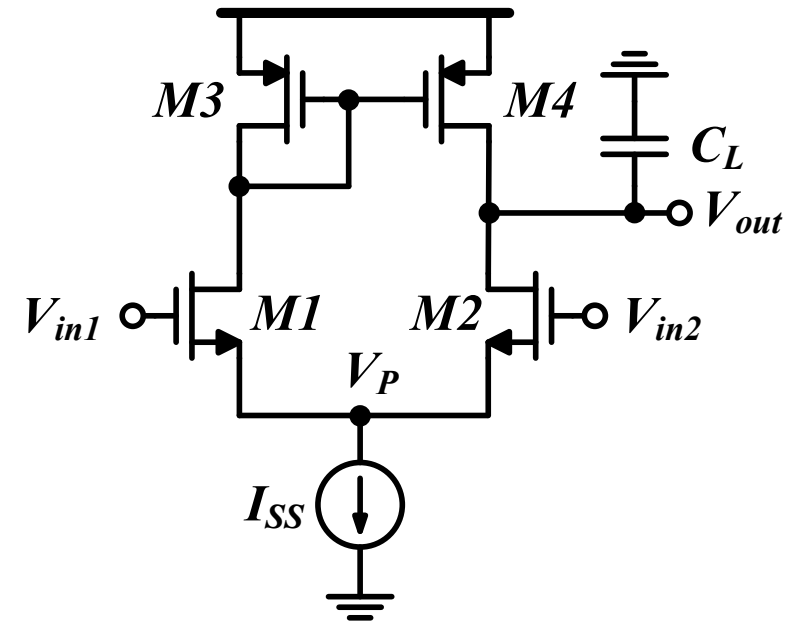

5T OTA


□ Fully differential?

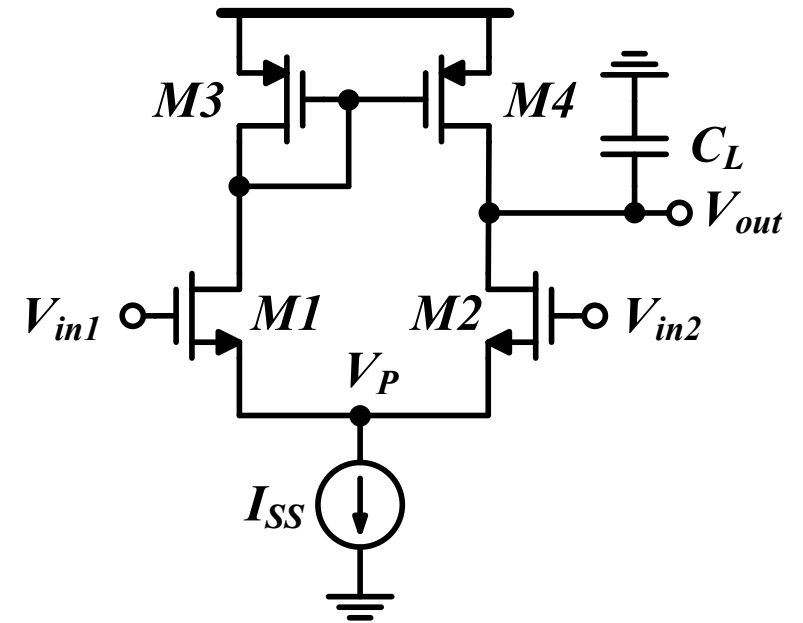

5T OTA


□ Fully differential with mismatch?

$$\begin{aligned} H(s) &= \frac{A_o/2}{1 + \frac{s}{\omega_{p1}}} + \frac{A_o/2}{1 + \frac{s}{\omega_{p1} + \Delta\omega}} \\ &= \frac{A_o \left\{ 1 + \frac{s}{2} \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p1} + \Delta\omega} \right) \right\}}{\left(1 + \frac{s}{\omega_{p1}} \right) \left(1 + \frac{s}{\omega_{p1} + \Delta\omega} \right)} \\ &= \frac{A_o \left(1 + \frac{s}{\omega_z} \right)}{\left(1 + \frac{s}{\omega_{p1}} \right) \left(1 + \frac{s}{\omega_{p1} + \Delta\omega} \right)} \end{aligned}$$

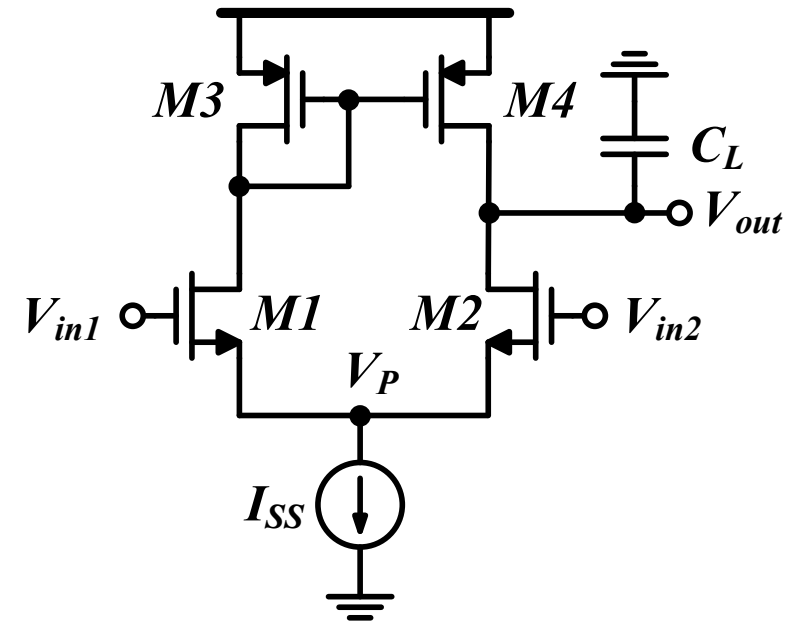

Telescopic Cascode

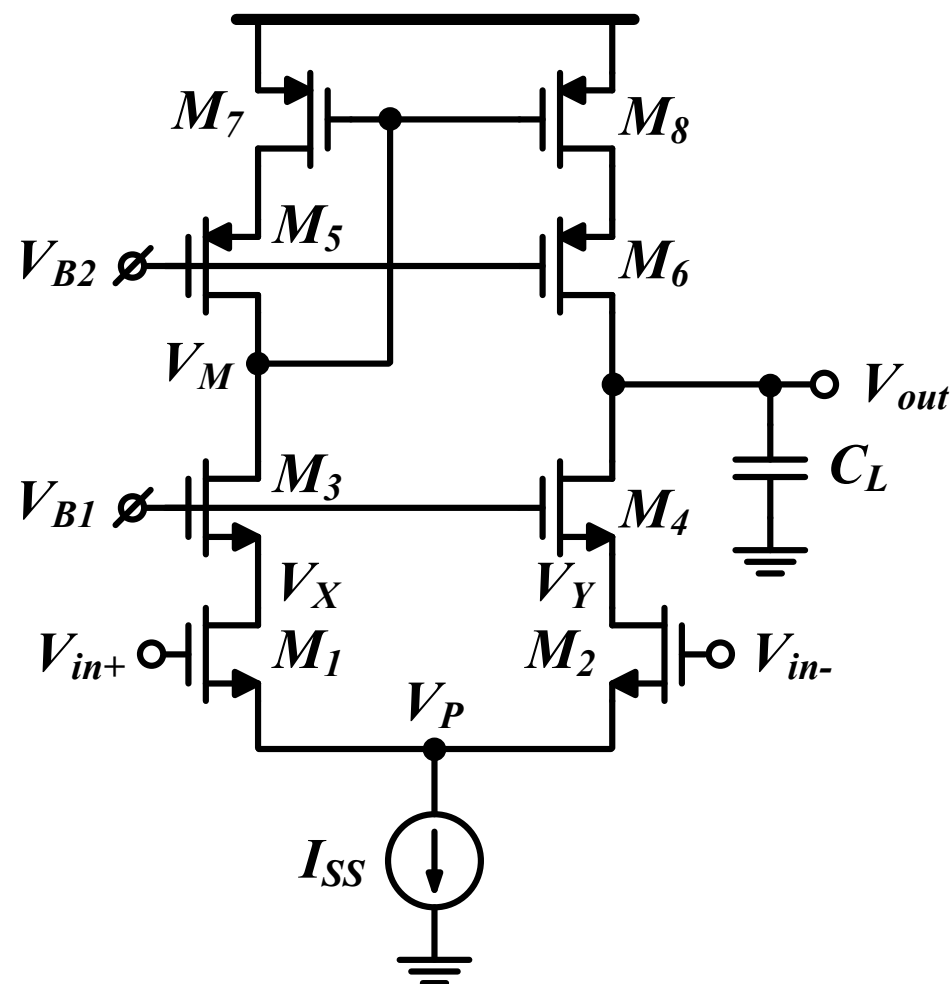- Higher DC gain, but limited swing and additional poles




Telescopic Cascode: Poles

- ❑ $\omega_{p1} \ll \omega_u < \omega_{p2}$
- ❑ The H.I.N. sets BW_{OL}

$$\omega_{p1} = \omega_{pout} = \frac{1}{R_{out}C_{out}}$$



- ❑ V_X and V_Y contribute a single pole
- ❑ Non-dominant poles considerations:
 - C_{gs} is larger than other caps
 - PMOS contributes larger capacitances (lower I_D/W)
- ❑ The first non-dominant pole (mirror node) sets the ultimate GBW
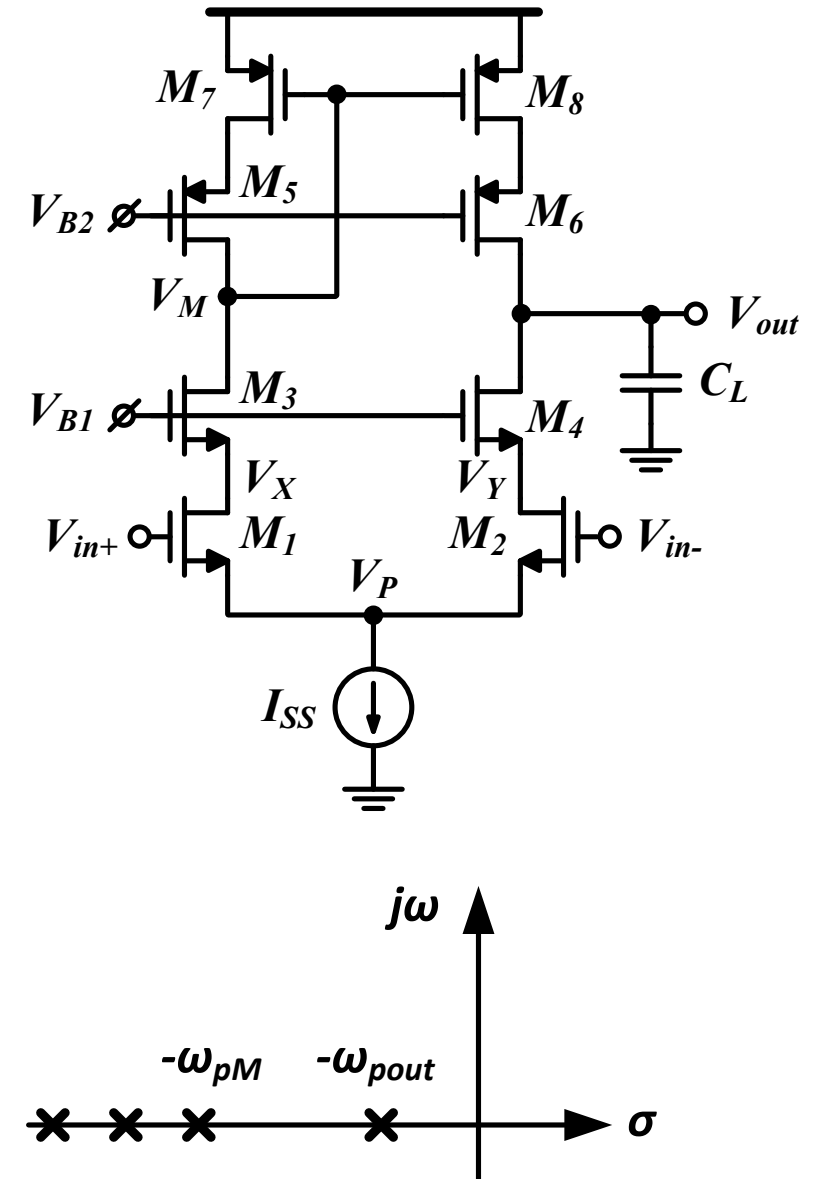
$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m7}}{C_M} \sim \frac{\omega_T}{4}$$



Folded Cascode

- ❑ Two possible implementations for SE output
- ❑ Compared to telescopic cascode:
 - More power ($\sim 2x$)
 - Lower gain ($r_{o1} || r_{o2}$)
 - More nodes/poles
 - More complex
 - But input and output ranges decoupled

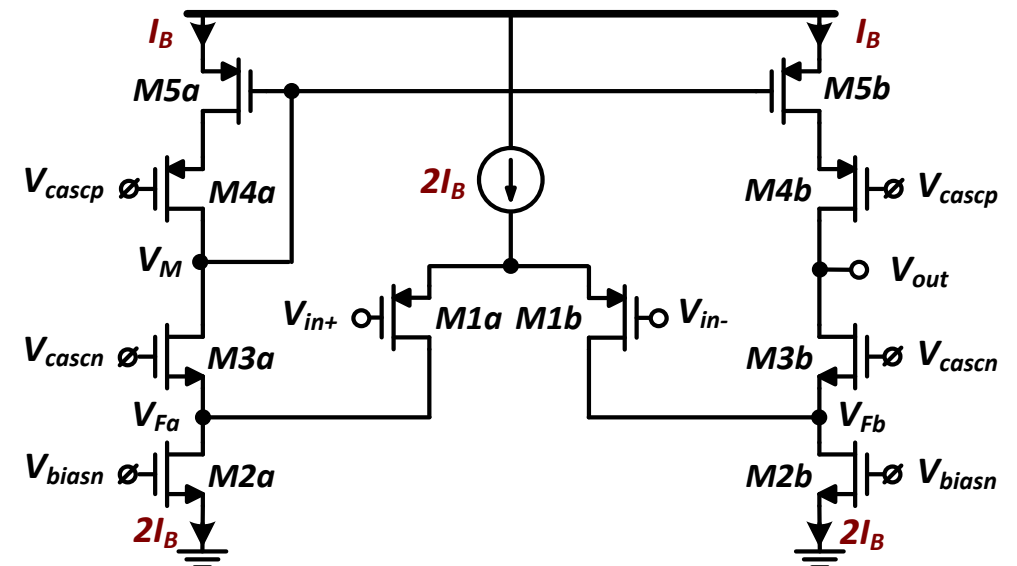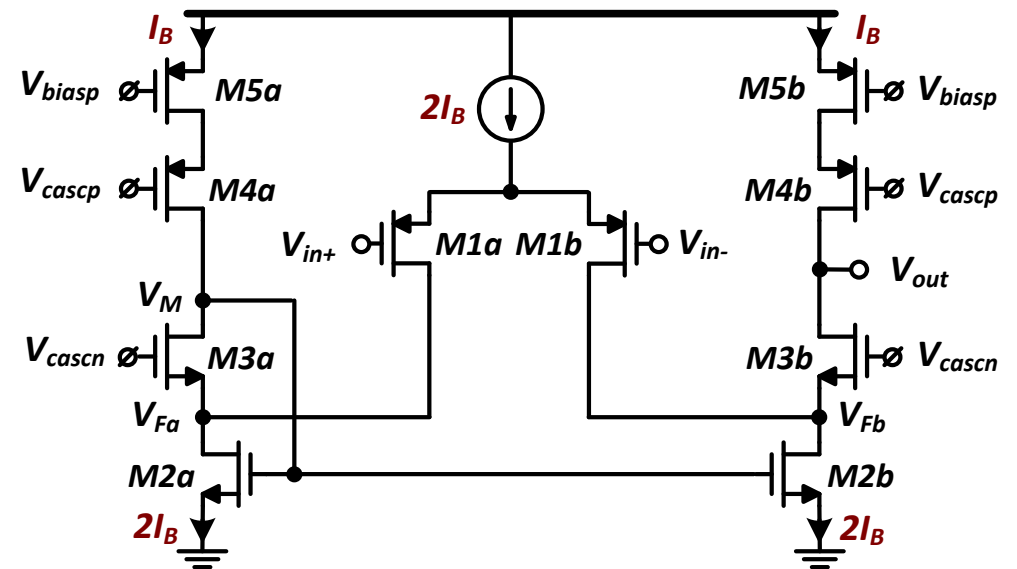

Folded Cascode: Poles

- $\omega_{p1} \ll \omega_u < \omega_{p2}$
- The H.I.N. sets BW_{OL}

$$\omega_{p1} = \omega_{pout} = \frac{1}{R_{out}C_{out}}$$

- The first non-dominant pole sets the ultimate GBW

- Mirror node (V_M)

$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m5}}{C_M}$$


- Or folding node (V_F)

$$\omega_{p2} = \omega_{pF} \approx \frac{g_{m3}}{C_F}$$

- V_{Fa} and V_{Fb} contribute a single pole



- Considerations:

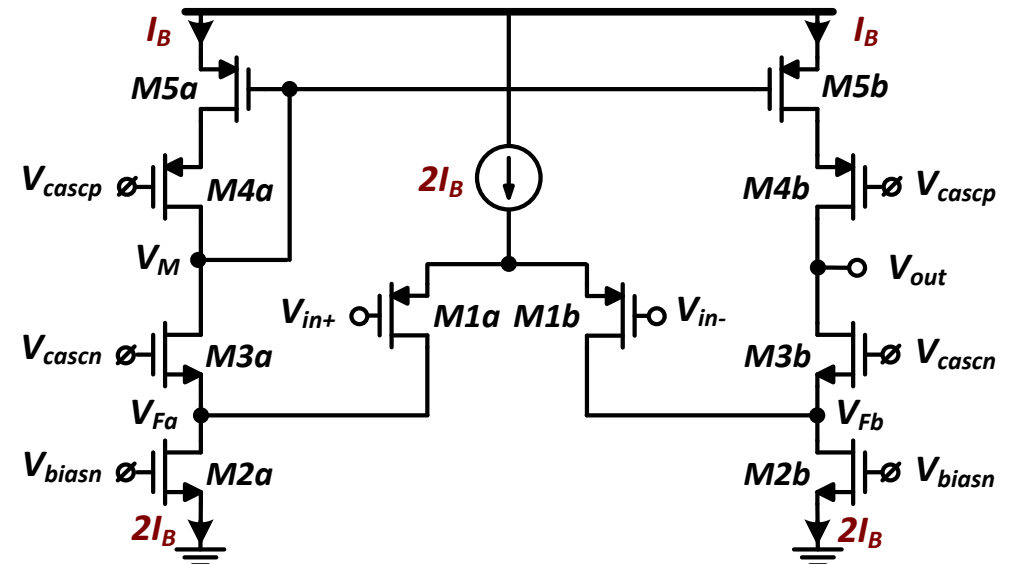- C_{gs} larger than other caps
- PMOS larger than NMOS
- M2 has large capacitance (double the current)





Single-Stage OTAs: Compensation

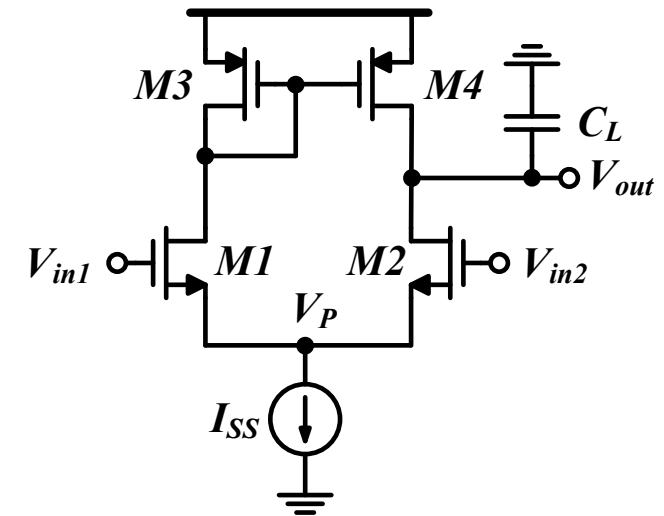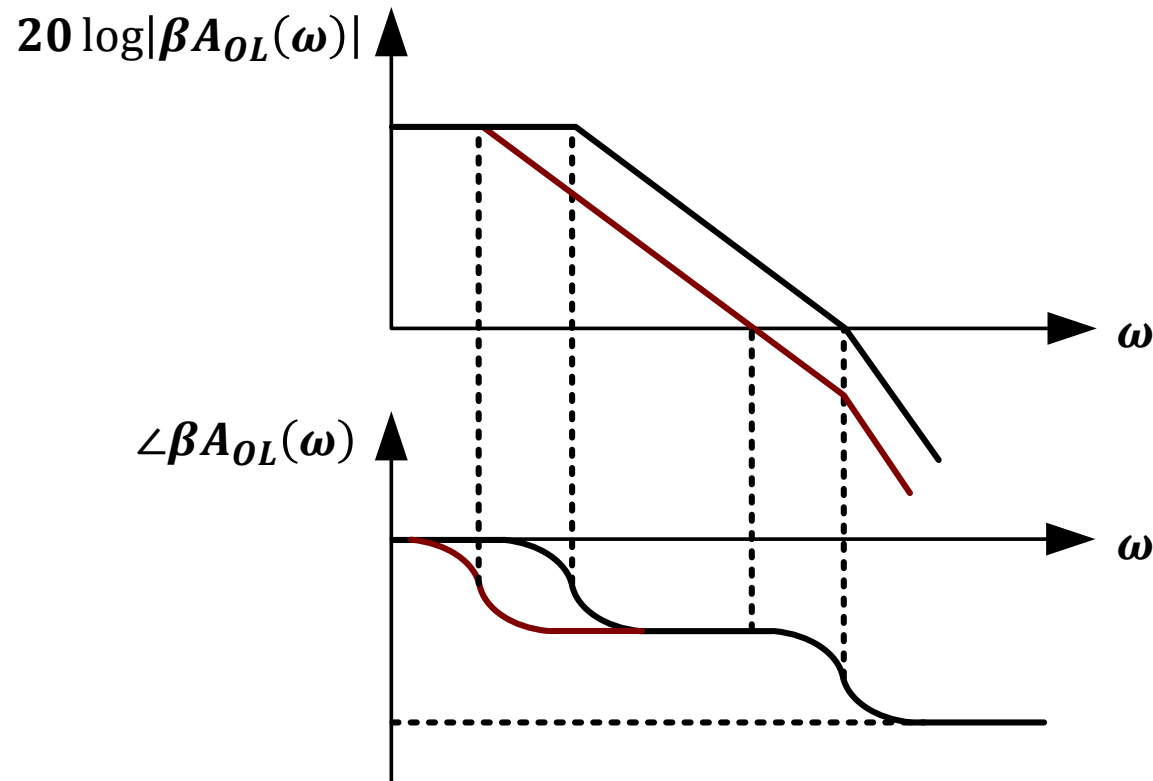- ❑ Push $G_X / \omega_u / \omega_{p1}$ **inwards**: lower GBW
 - Increase C_L
 - **Single-stage OTAs are compensated by large load capacitance**



Single-Stage OTAs: Compensation

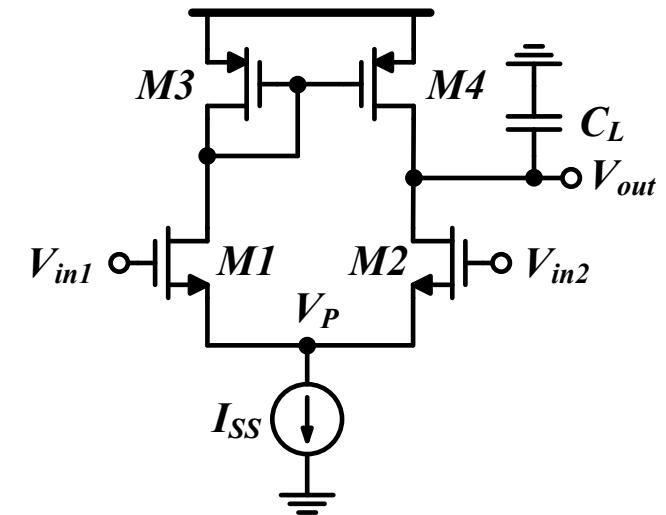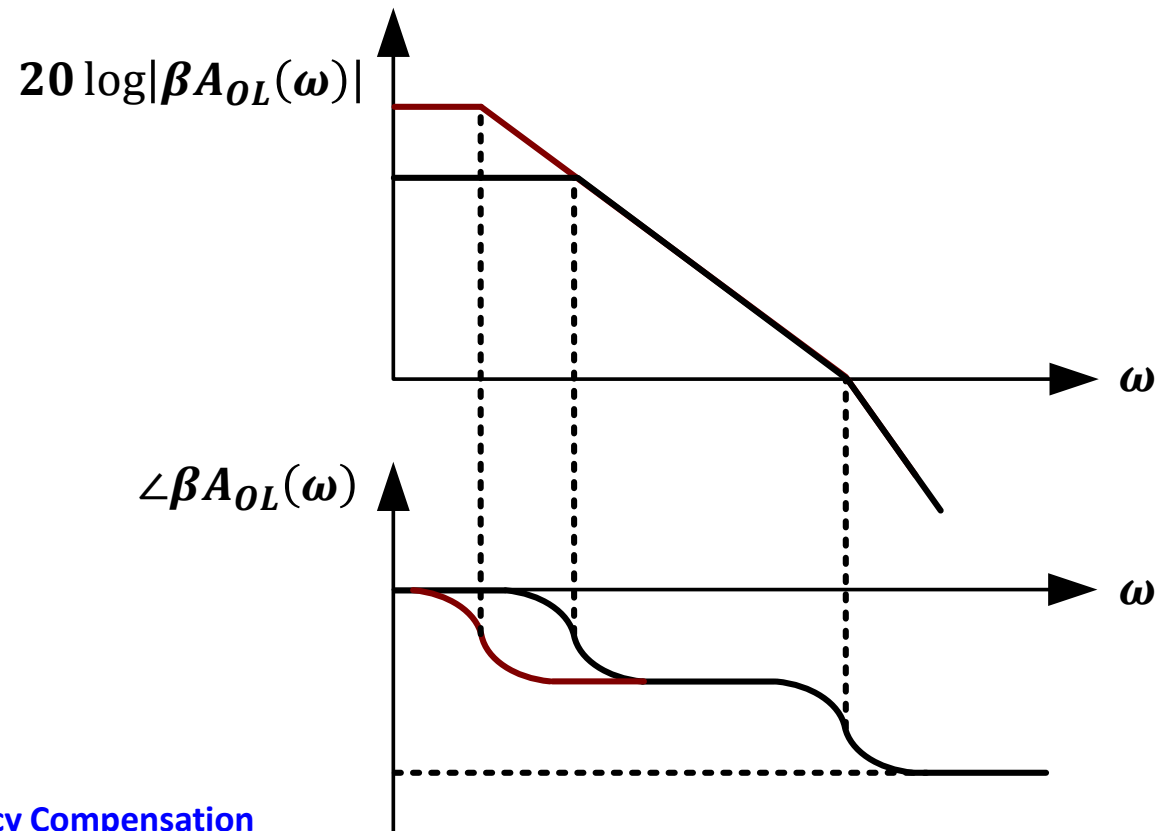- ❑ Push $G_X / \omega_u / \omega_{p1}$ **inwards**: lower GBW
 - Increase C_L
 - **Single-stage OTAs are compensated by large load capacitance**
- ❑ Increasing R_{out} does not affect PM




Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero


Two-Stage OTA

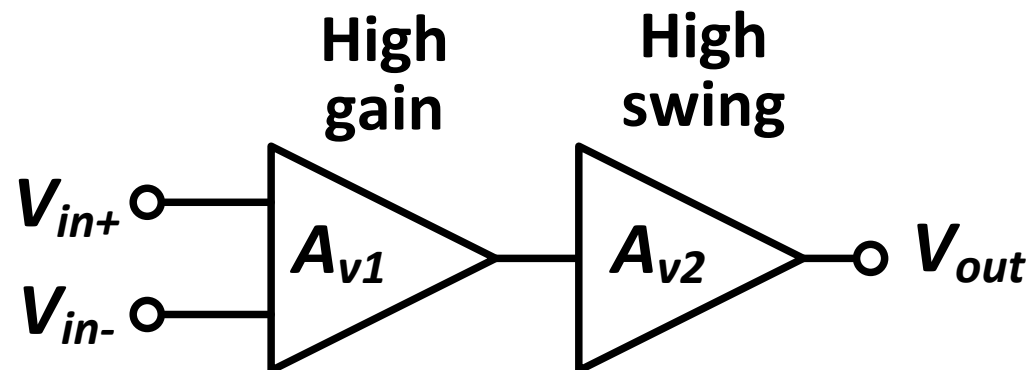- ❑ Isolates the gain and swing requirements
 - But much more power consumption
 - And complicates stability requirements
- ❑ Three-stage OTA exists, but quite difficult to stabilize
- ❑ First stage can be 5T-OTA or cascode
- ❑ Second stage is typically a simple common-source
 - Allows maximum output swing



Two-Stage OTA: Poles

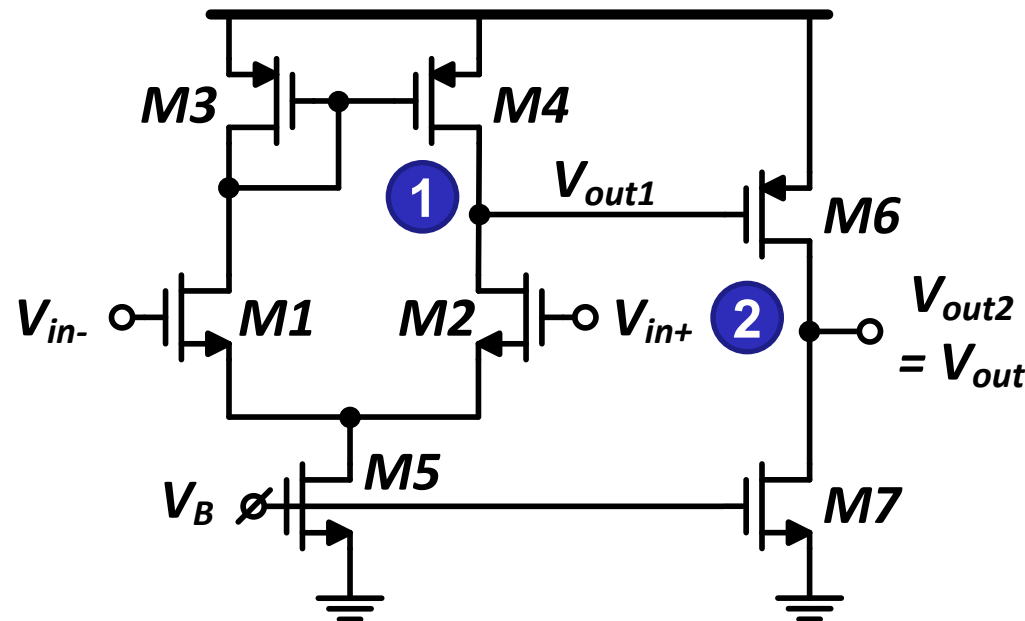- ❑ Two gain stages $\rightarrow$ Two H.I.N.s
 - Two dominant poles!
- ❑ Internal pole: $\omega_{p1} = \frac{1}{R_{out1}C_1}$
- ❑ Output pole: $\omega_{p2} = \frac{1}{R_{out2}C_2}$




Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

Two-Stage OTA: Miller Compensation

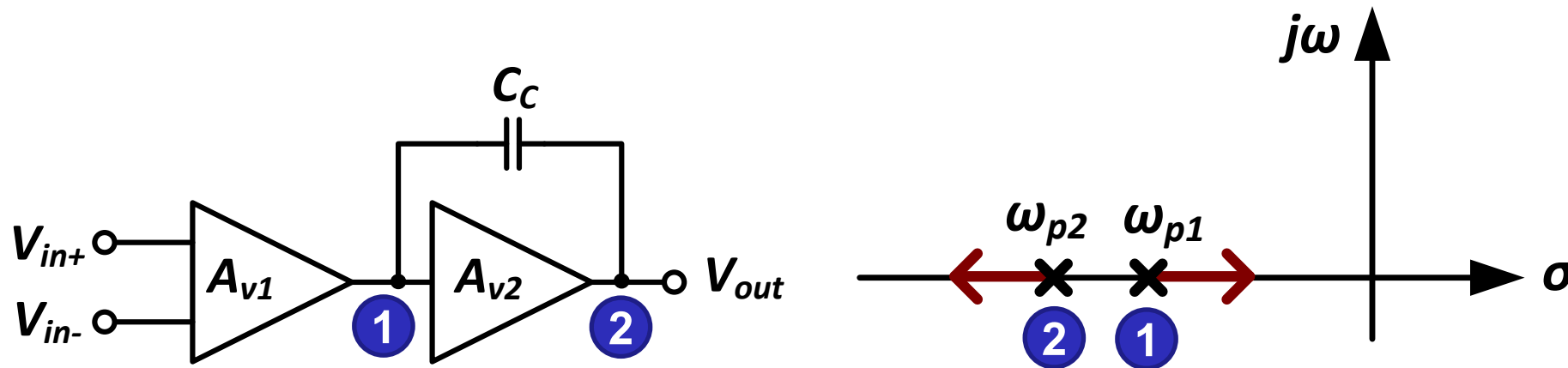- ❑ Exploit Miller capacitance multiplication
- ❑ Pole splitting
 - Push ω_{p1} inwards $\rightarrow$ push GX inwards
 - Push ω_{p2} outwards $\rightarrow$ push PX outwards



CS HFR: Reminder

❑ Surprisingly, exact analysis gives a quite complex expression

- See [Johns & Martin 2012] or [Razavi 2017]

❑ If dominant pole approximation is applied

$$\omega_{pd} \approx \frac{1}{b_1} = \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})] + R_{out}(C_{out} + C_{gd})}$$

- Same result as OCTC (both based on same approximation)

❑ Additionally, dominant pole approx gives an expression for ω_{pnd}

$$\omega_{pnd} \approx \frac{1}{b_2 \omega_{p1}} = \frac{b_1}{b_2} = \frac{g_m C_{gd}}{C_{gd}(C_{gs} + C_{out}) + C_{gs} C_{out}}$$

- If a large cap is connected parallel to C_{gd} : $\omega_{pnd} \approx \frac{g_m}{C_{gs} + C_{out}}$
 - Can be derived intuitively without analysis (how?)

Two-Stage OTA: Miller Compensation



❑ Before compensation

$$\omega_{p1} = \frac{1}{R_{out1}C_1} \quad \& \quad \omega_{p2} = \frac{1}{R_{out2}C_2}$$

❑ After compensation: Pole splitting

$$\omega_{p1} \approx \frac{1}{R_{out1}[(G_{m2}R_{out2})C_C + C_1] + R_{out2}(C_2 + C_C)} \approx \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$
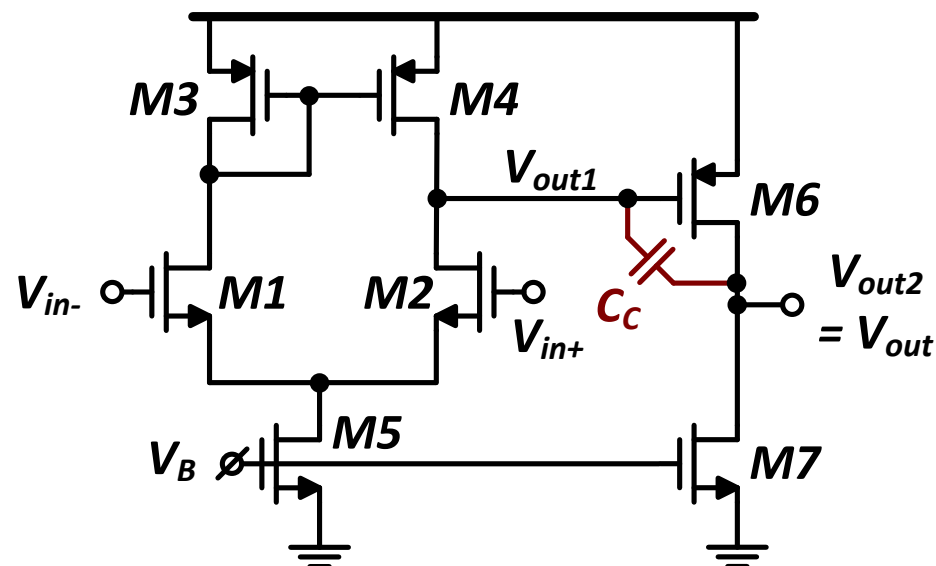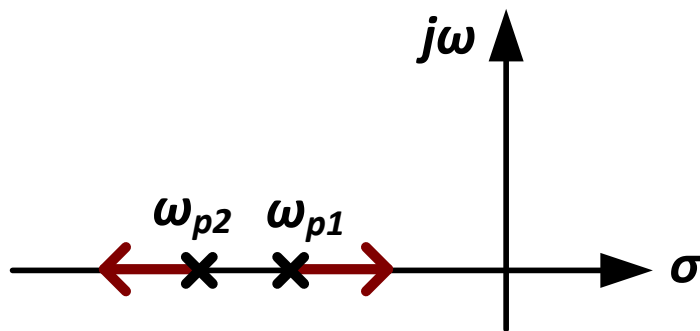
$$\omega_{p2} \approx \frac{G_{m2}C_C}{C_C(C_1 + C_2) + C_1C_2} \approx \frac{G_{m2}}{C_1 + C_2}$$



Stability Requirement: ω_u and ω_{p2}

$$\omega_{p1} \approx \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$

$$\omega_{p2} \approx \frac{G_{m2}}{C_1 + C_2} \approx \frac{G_{m2}}{C_L}$$


$$GBW \approx G_{m1}R_{out1}G_{m2}R_{out2} \cdot \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$

$$GBW = \omega_u \approx \frac{G_{m1}}{C_C}$$

□ For critical damped response: $\zeta = 1$,

$Q = 0.5$, and $PM \approx 76^\circ$
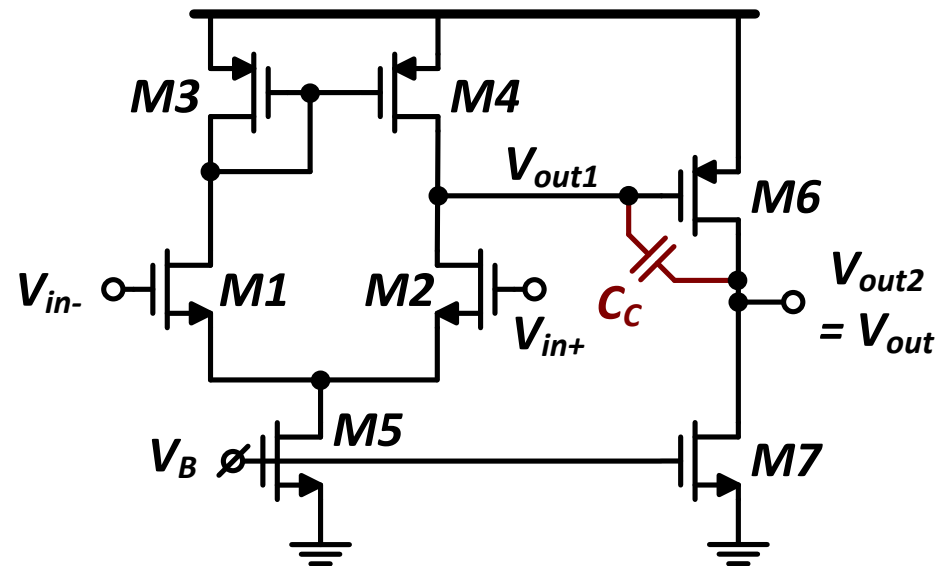
$$\omega_{p2} \approx 4\omega_u \rightarrow \frac{G_{m2}}{C_L} \approx \frac{4G_{m1}}{C_C}$$



Bias Current in 1st and 2nd Stages

$$\frac{G_{m2}}{C_L} \approx \frac{4G_{m1}}{C_C}$$


- Assume $C_L = 4pF$ and $C_C = C_L/2 = 2pF$

$$\frac{G_{m2}}{G_{m1}} = 4 \times \frac{4}{2} = 8$$

- If both stages use the same gm/ID
 - Note that $I_{B1} = 2 \times I_{D1,2}$



$$\frac{I_{B2}}{I_{B1}} = 4$$

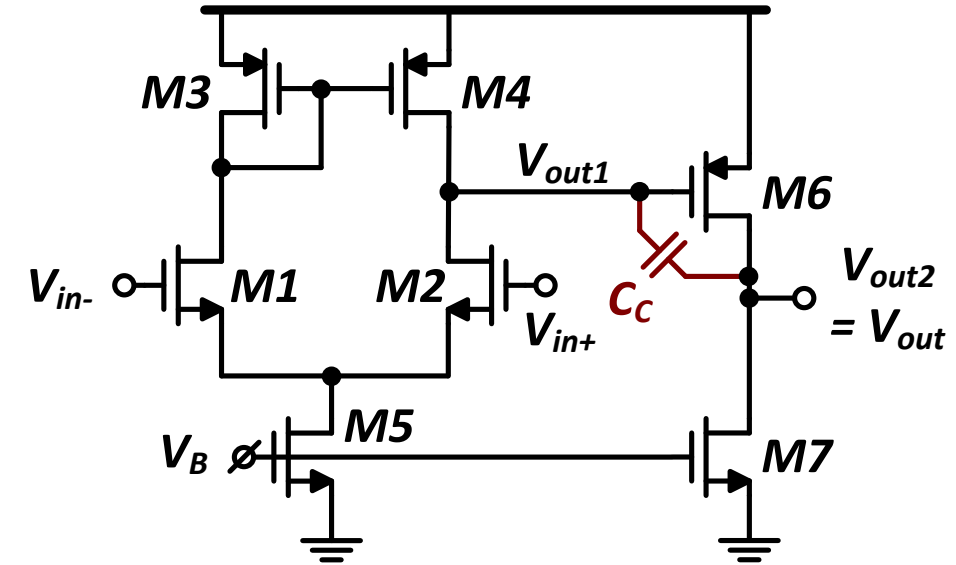- 80% of the power is consumed in the second stage to achieve stability
 - 80% of bias current do not contribute (directly) to GBW
 - Miller OTA is very energy inefficient!





Miller OTA: Pole Splitting with C_C

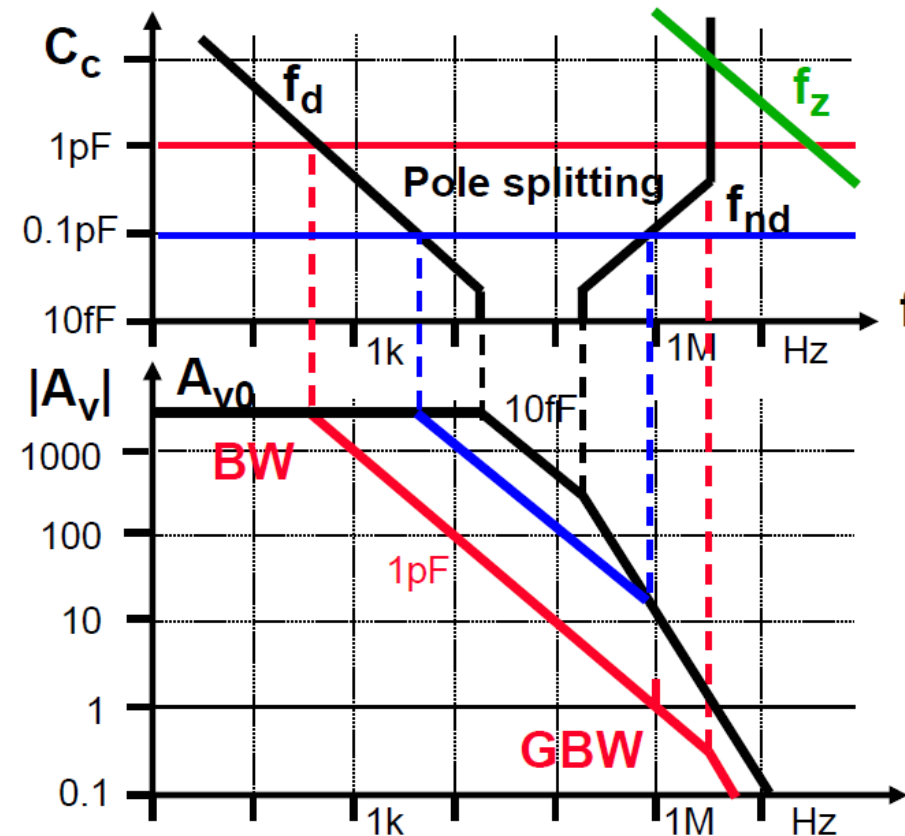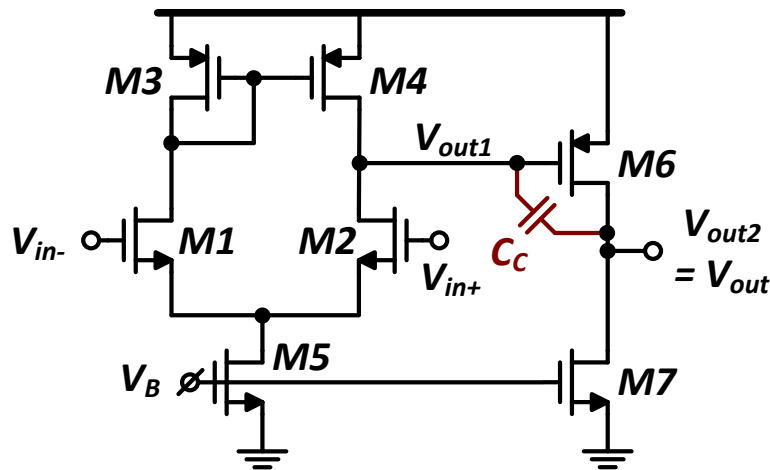- ❑ Too large C_C does not give more pole splitting: just smaller GBW
 - Usually we choose $C_1 < C_C < C_L$
 - Reasonable starting point: $C_C \approx (0.3 \rightarrow 0.5) \times C_L$




Miller OTA: Pole Splitting with G_{m2}

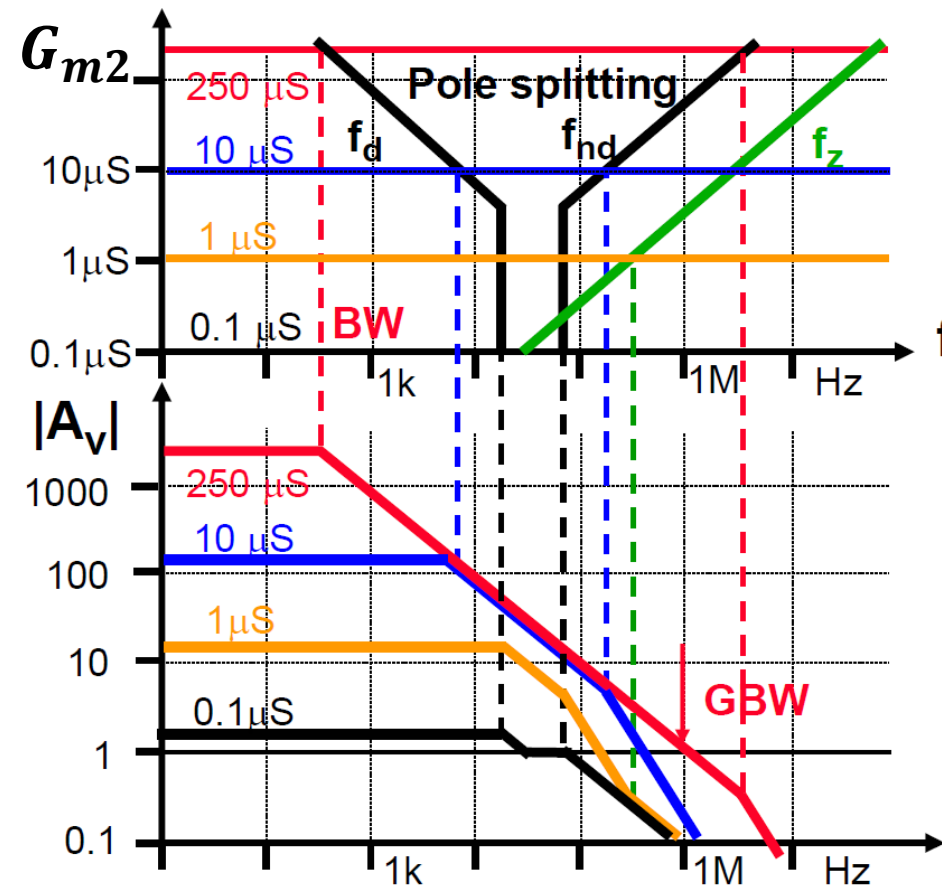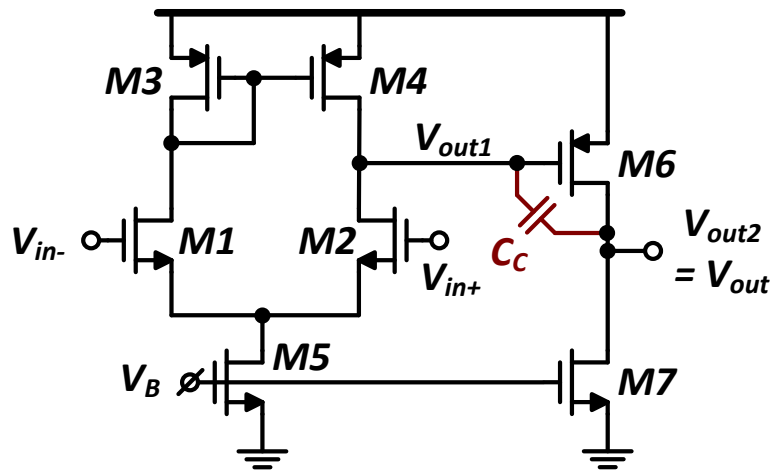- Increasing G_{m2} works even better than increasing C_c
 - But more power consumption in the 2nd stage



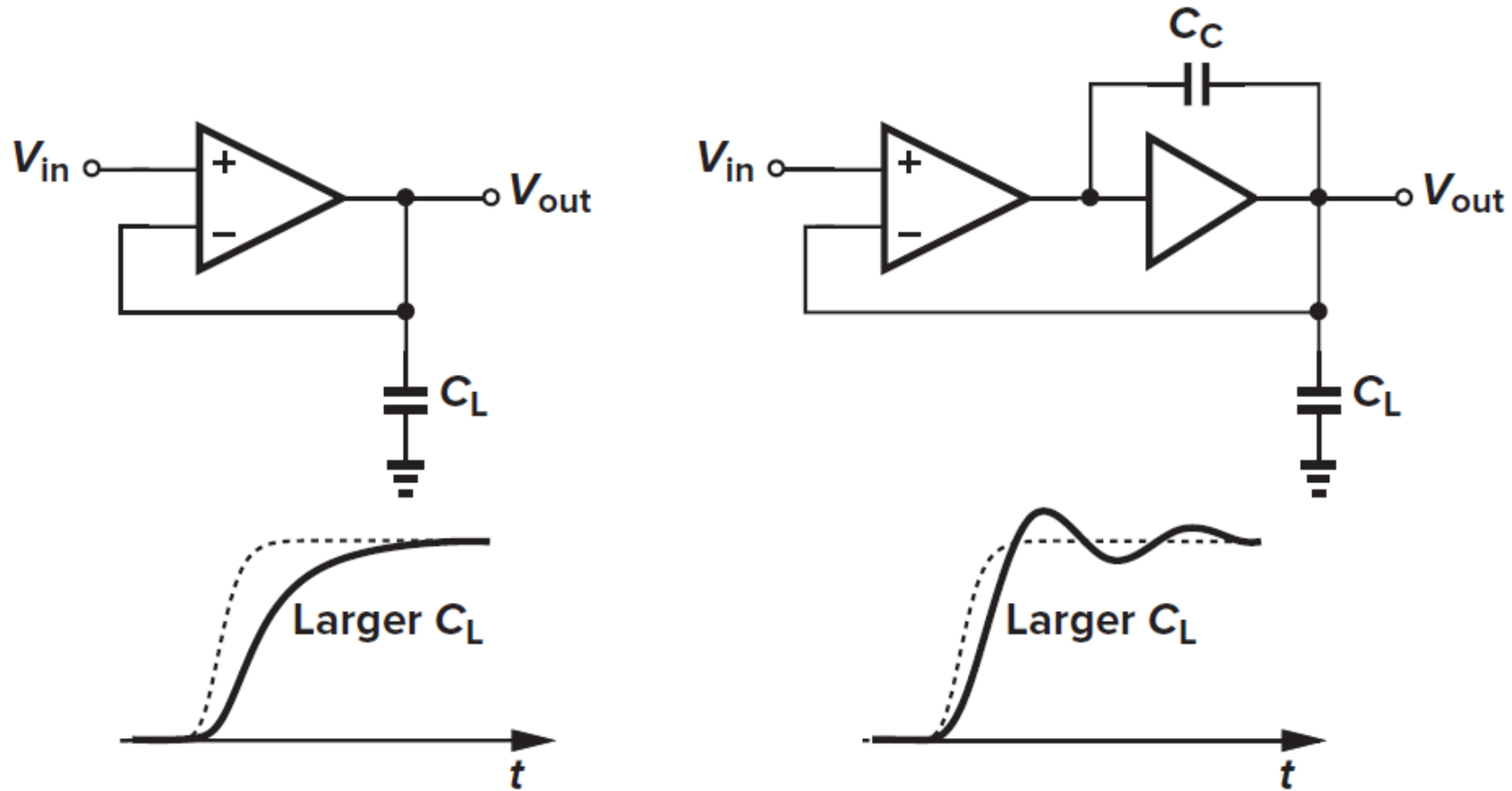Single vs Two-Stage OTA: Sensitivity to C_L



Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
 - Miller compensation
 - The feedforward zero

The Feedforward Zero: **Reminder**

□ $v_{out} = 0 \rightarrow i_{out} = 0$



□ $v_{in} s C_F = -G_m v_{in}$

$$s_z = -\frac{G_m}{C_F}$$

□ LHP zero if G_m is +ve (e.g. CD)

□ **RHP zero if G_m is -ve (e.g. CS)**

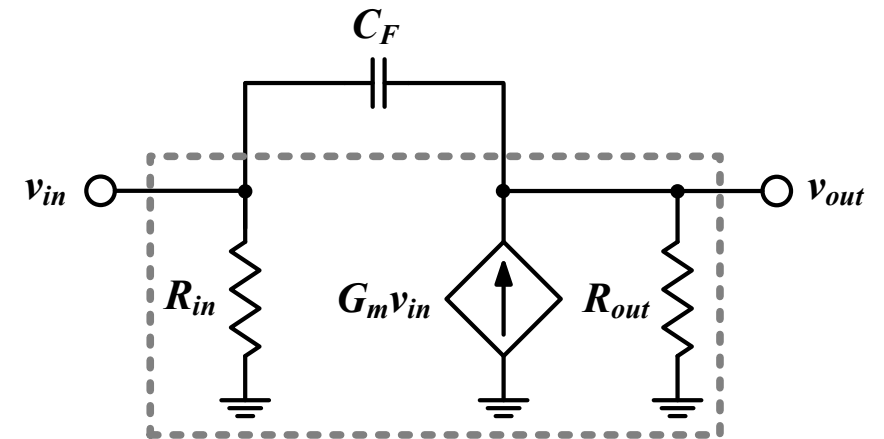
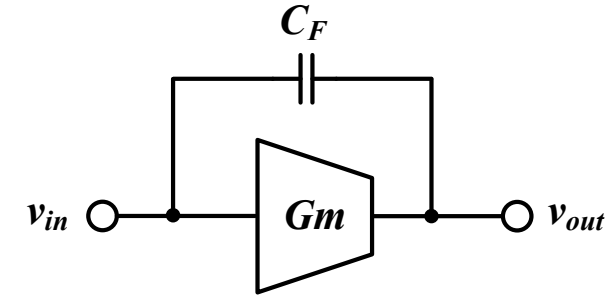
- Mag inc and phase drops
- Very bad for FB loop stability



Miller OTA: The RHP Zero

- ❑ RHP zero is bad for both magnitude and phase
 - Pushes GX outwards and pushes PX inwards
 - Increasing C_C may hurt stability!
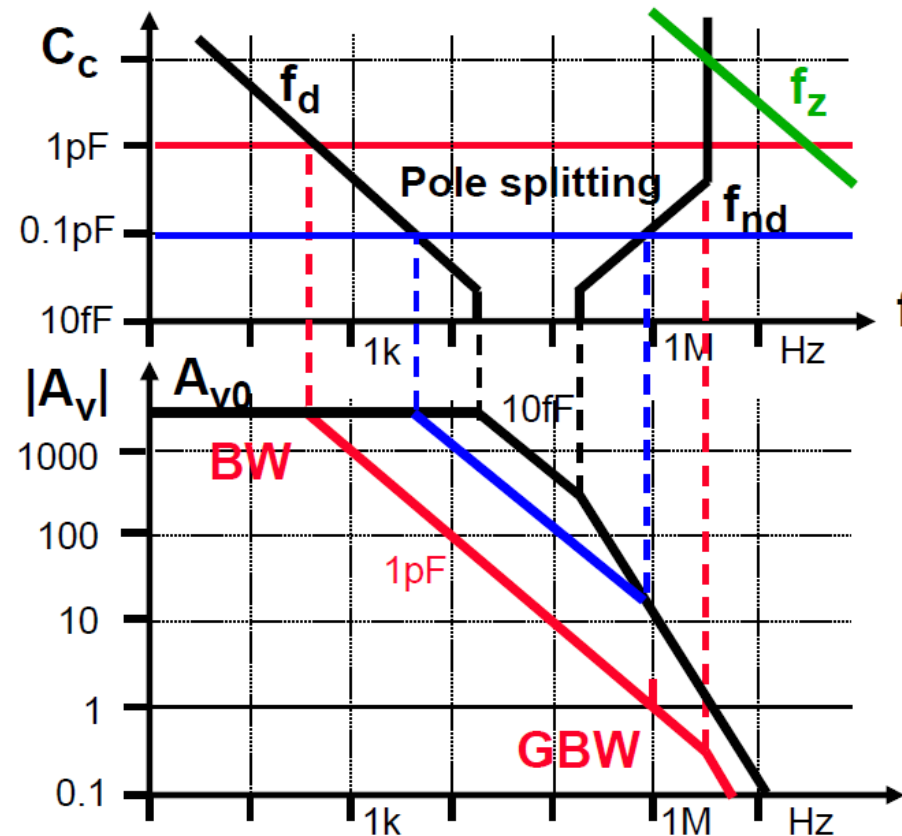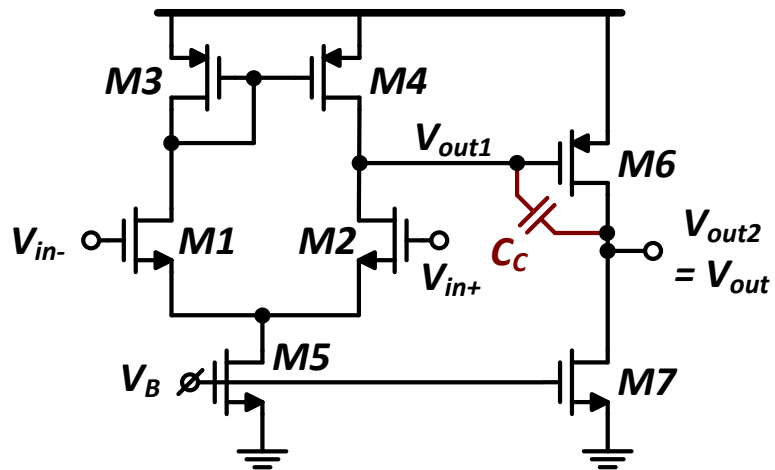
$$\omega_z = \frac{g_{m6}}{C_C + C_{gd}} \approx \frac{G_{m2}}{C_C}$$




Handling the RHP Zero

- ❑ Add a resistance to control the value of the zero (other tricks exist)

$$\frac{v_{out1}}{R_Z + \frac{1}{s_Z C_C}} = g_{m6} v_{out1}$$
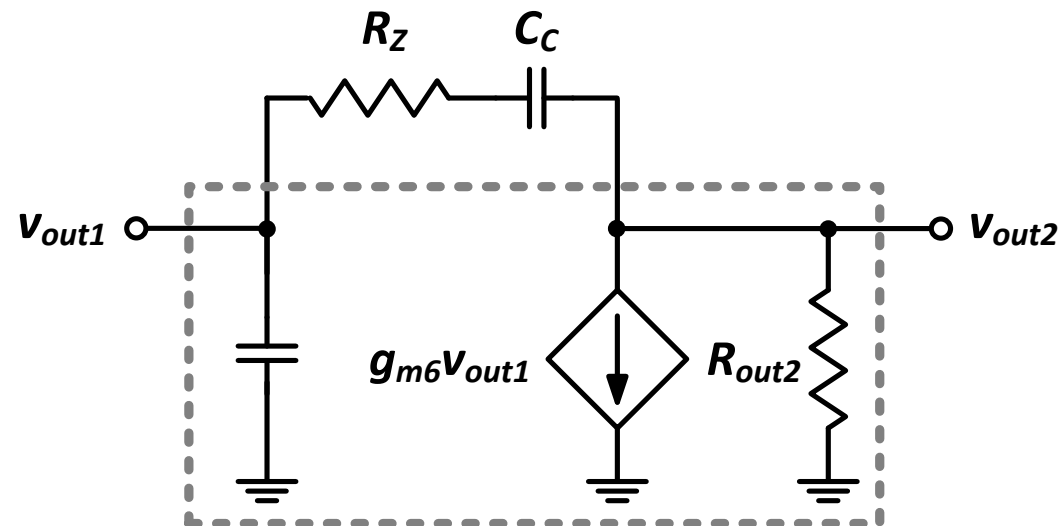
$$s_Z = \frac{1}{C_C \left(\frac{1}{g_{m6}} - R_Z \right)}$$



Miller Zero Placement

- ❑ Place the zero at ∞

$$\omega_z = \frac{1}{C_C \left(\frac{1}{G_{m2}} - R_Z \right)} \rightarrow R_Z = \frac{1}{G_{m2}}$$


- ❑ Some designers try to move the zero to the LHP to cancel the first non-dominant pole and/or improve the PM

$$\frac{1}{C_C \left(R_Z - \frac{1}{G_{m2}} \right)} = \frac{G_{m2}}{C_L} \rightarrow R_Z = \frac{C_L + C_C}{G_{m2} C_C}$$

- Practically never achieved due to variations
- Actually does not lead to faster response (why?)
- ❑ Pushing the LHP zero to lower frequencies is even worse
 - Very poor settling time (a.k.a. pole-zero doublet)
 - Noise amplification


Miller OTA Behavioral Model

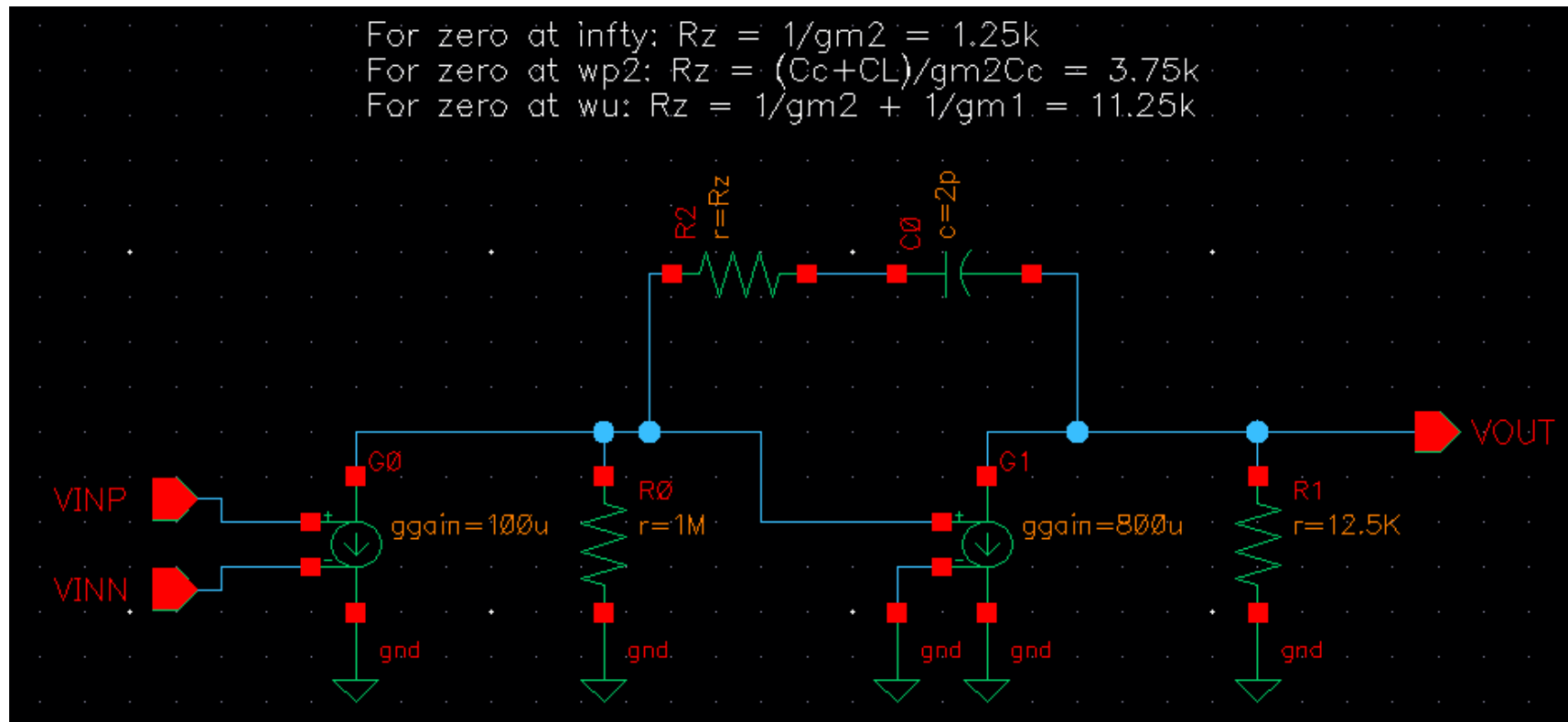- Try three different strategies for Miller zero placement
 - ∞
 - Cancel ω_{p2}
 - At ω_u (this is a designer mistake rather than a valid strategy!)





TB for LG and Step Response

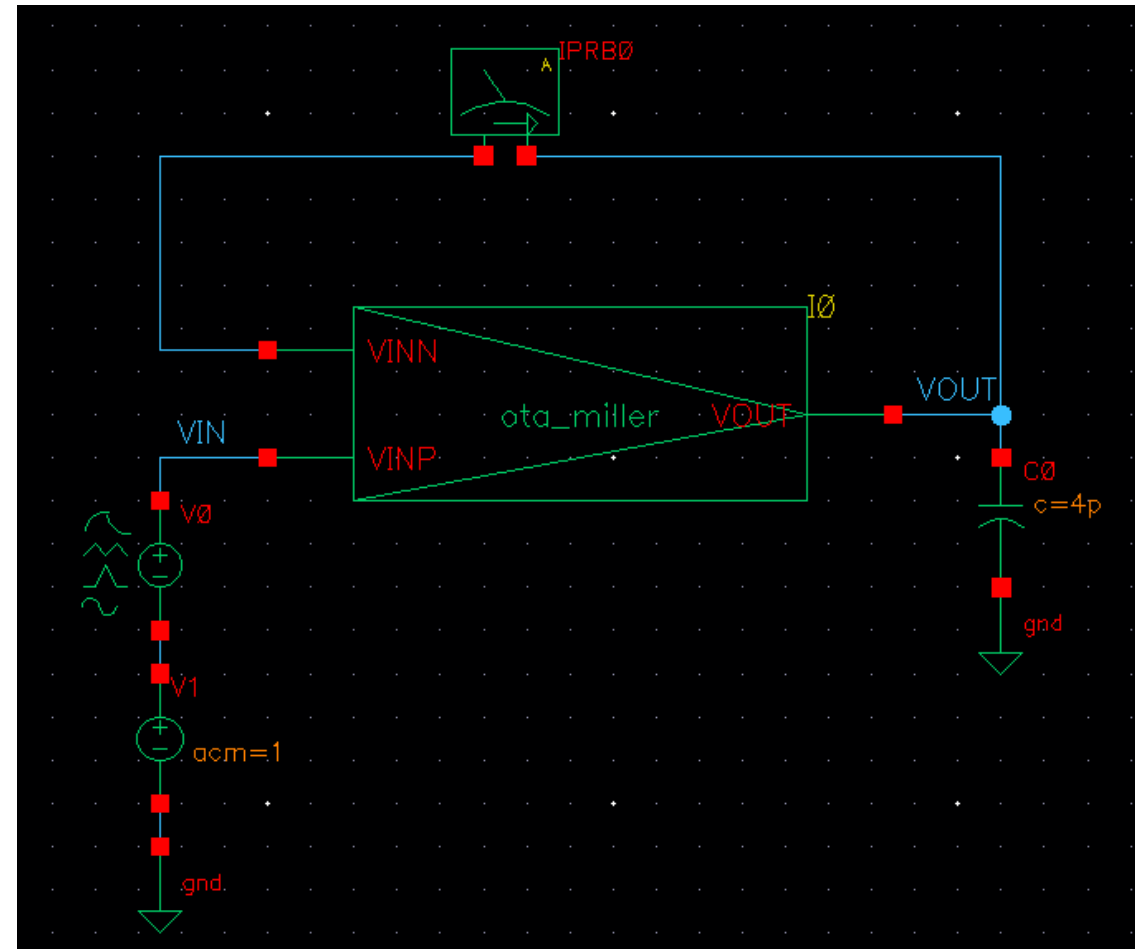
- Verify stability, ac response, and transient response in unity-gain buffer configuration.



LG and Step Response

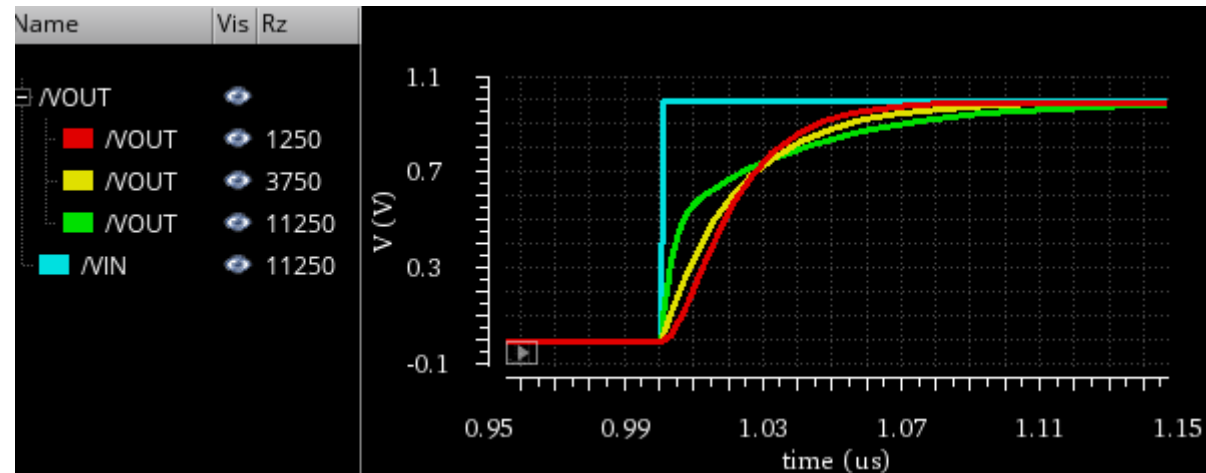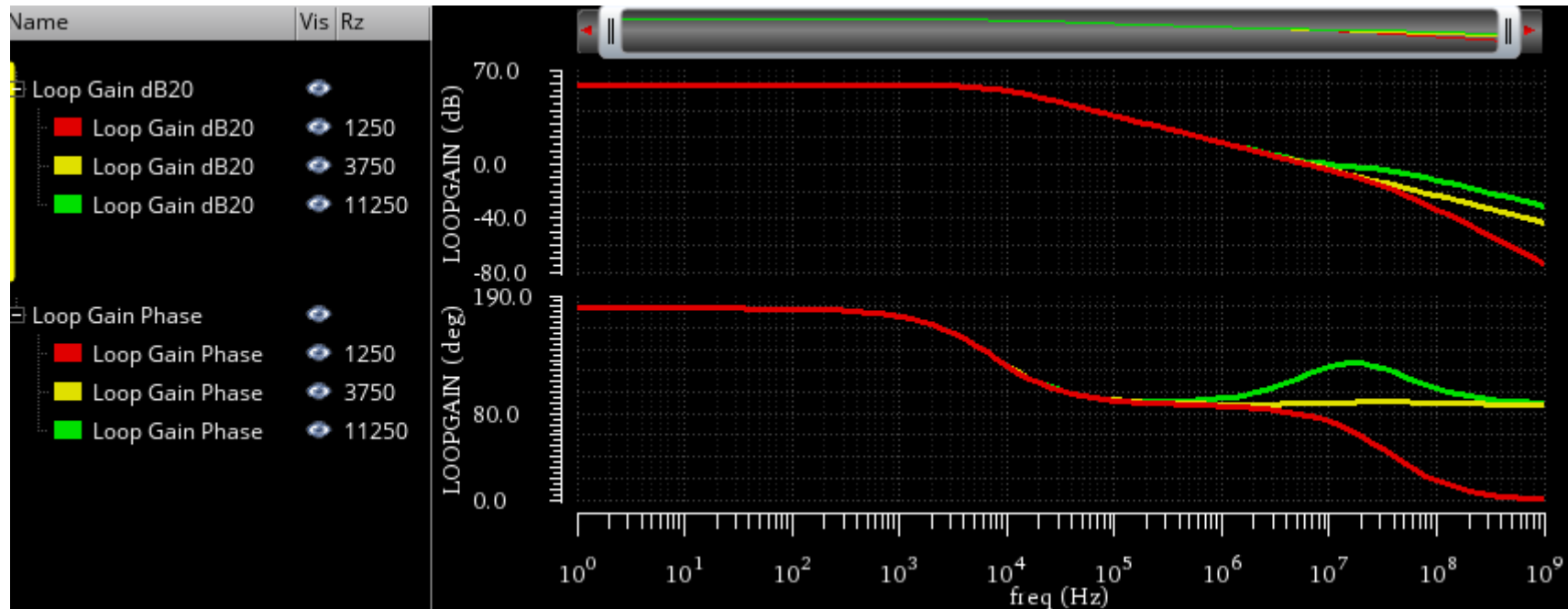


LG and CL Gain

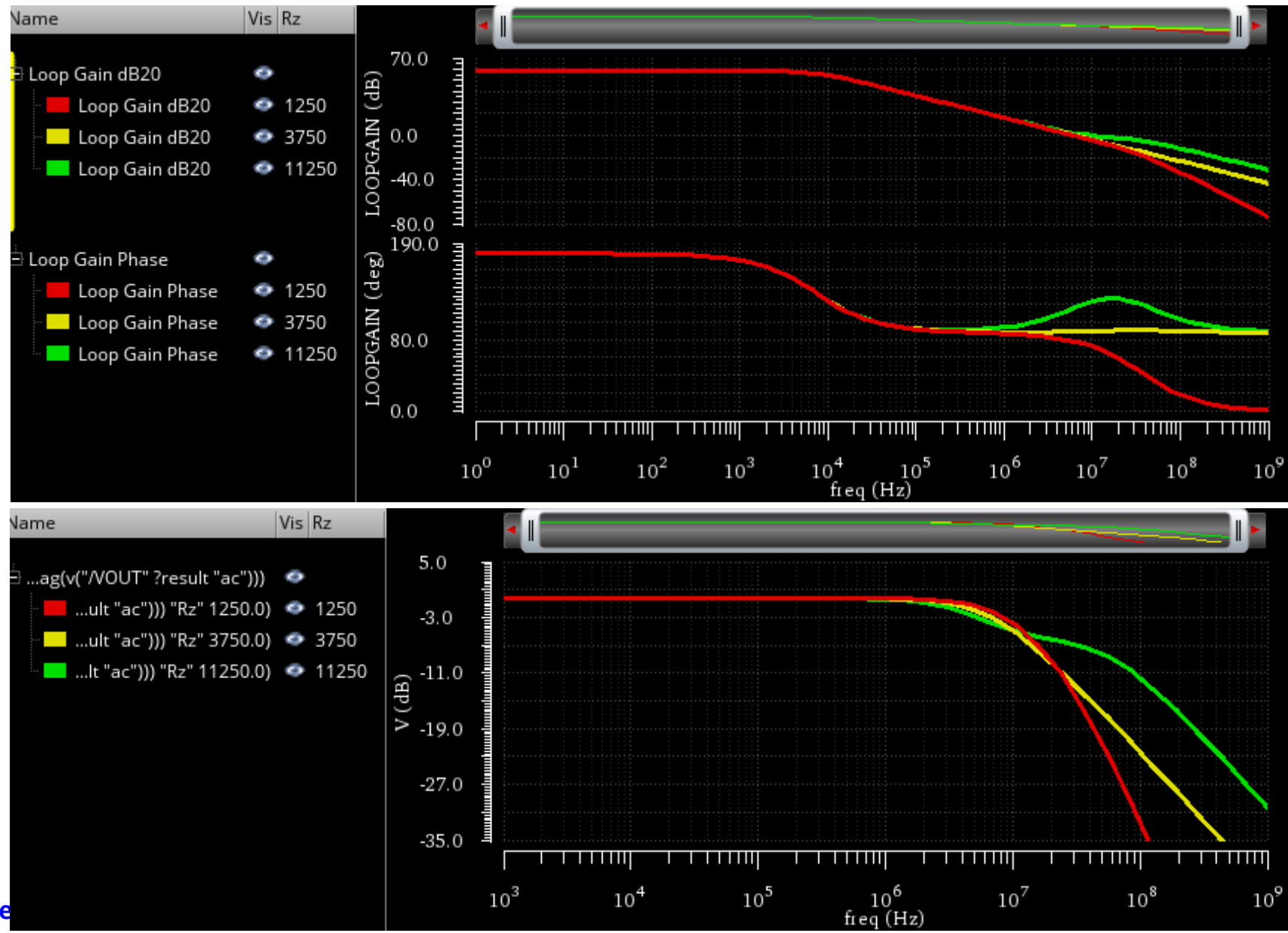

R_Z Implementation

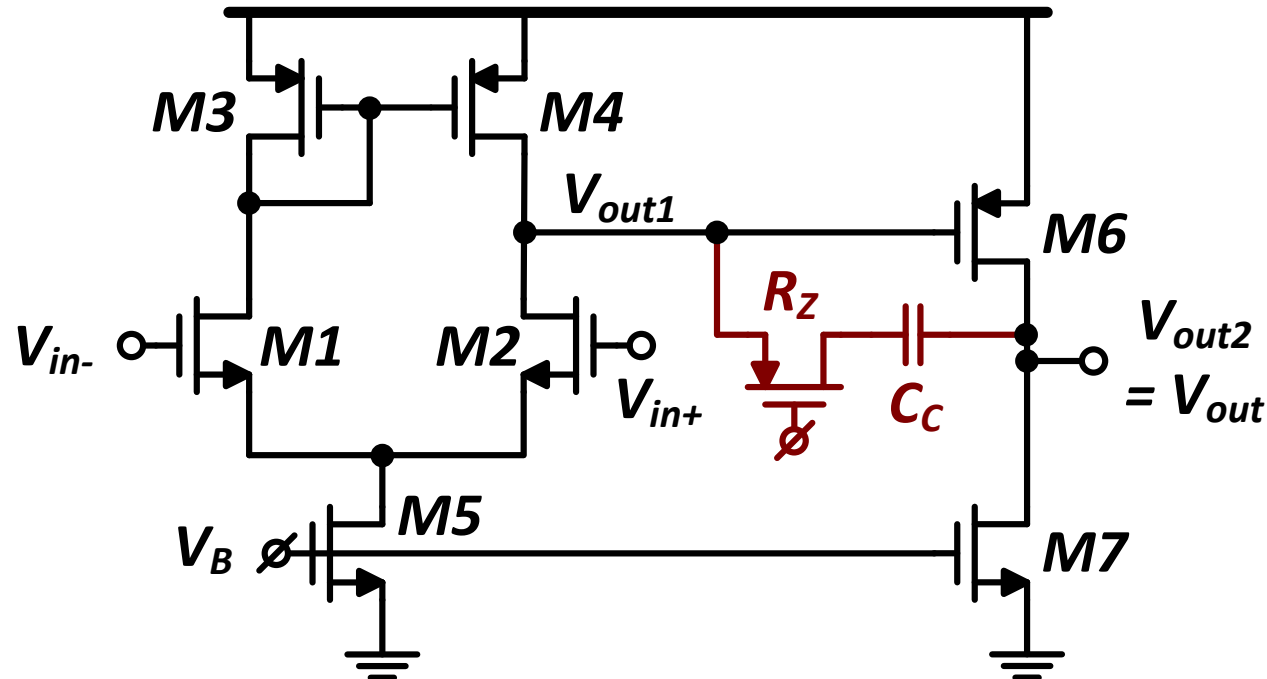- R_Z can be implemented as a simple resistor or using a transistor in the linear region
 - Clever biasing can make it track variations (maintain $R_Z \approx \frac{1}{g_{m6}}$)
 - Why R_Z is implemented as PMOS?



Thank you!

References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” Oxford University Press, 7th ed., 2015
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017.
- ❑ W. Sansen, “Analog design essentials,” Springer, 2006.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012.
- ❑ B. Murmann, EE214 Course Reader, Stanford University.